
Practical Electrical Engineering

Sergey N. Makarov • Reinhold Ludwig
Stephen J. Bitar

Practical Electrical Engineering

 Springer

Sergey N. Makarov
ECE Department
Worcester Polytechnic Institute
Worcester, Washington, USA

Reinhold Ludwig
ECE Department
Worcester Polytechnic Institute
Worcester, Massachusetts, USA

Stephen J. Bitar
Worcester Polytechnic Institute
Worcester, Massachusetts, USA

ISBN 978-3-319-21172-5 ISBN 978-3-319-21173-2 (eBook)
DOI 10.1007/978-3-319-21173-2

Library of Congress Control Number: 2015950619

© Springer International Publishing Switzerland 2016

This work is subject to copyright. All rights are reserved by the Publisher, whether the whole or part of the material is concerned, specifically the rights of translation, reprinting, reuse of illustrations, recitation, broadcasting, reproduction on microfilms or in any other physical way, and transmission or information storage and retrieval, electronic adaptation, computer software, or by similar or dissimilar methodology now known or hereafter developed.

The use of general descriptive names, registered names, trademarks, service marks, etc. in this publication does not imply, even in the absence of a specific statement, that such names are exempt from the relevant protective laws and regulations and therefore free for general use.

The publisher, the authors and the editors are safe to assume that the advice and information in this book are believed to be true and accurate at the date of publication. Neither the publisher nor the authors or the editors give a warranty, express or implied, with respect to the material contained herein or for any errors or omissions that may have been made.

Printed on acid-free paper

This Springer imprint is published by Springer Nature
The registered company is Springer International Publishing AG Switzerland

To Antonina, Margot, and Juliette

Contents

1	From Physics to Electric Circuits	1
1.1	Electrostatics of Conductors	3
1.1.1	Charges, Coulomb Force, and Electric Field	3
1.1.2	Electric Potential and Electric Voltage	4
1.1.3	Electric Voltage Versus Ground	5
1.1.4	Equipotential Conductors	7
1.1.5	Use of Coulomb’s Law to Solve Electrostatic Problems	9
1.2	Steady-State Current Flow and Magnetostatics	11
1.2.1	Electric Current	11
1.2.2	Difference Between Current Flow Model and Electrostatics	11
1.2.3	Physical Model of an Electric Circuit	13
1.2.4	Magnetostatics and Ampere’s Law	14
1.2.5	Origin of Electric Power Transfer	16
1.3	Hydraulic and Fluid Mechanics Analogies	18
1.3.1	Hydraulic Analogies in the DC Steady State	18
1.3.2	Analogies for Alternating-Current (AC) Circuits	19
1.3.3	Analogies for Semiconductor Circuit Components	20

Part I DC Circuits: General Circuit Theory—Operational Amplifier

2	Major Circuit Elements	29
2.1	Resistance: Linear Passive Circuit Element	31
2.1.1	Circuit Elements Versus Circuit Components	31
2.1.2	Resistance	31
2.1.3	v - i Characteristic of the Resistance: Open and Short Circuits	34
2.1.4	Power Delivered to the Resistance	35
2.1.5	Finding Resistance of Ohmic Conductors	36

Contents

2.1.6	Application Example: Power Loss in Transmission Wires and Cables	39
2.1.7	Physical Component: Resistor	41
2.1.8	Application Example: Resistive Sensors	42
2.2	Nonlinear Passive Circuit Elements	46
2.2.1	Resistance as a Model for the Load	46
2.2.2	Nonlinear Passive Circuit Elements	47
2.2.3	Static Resistance of a Nonlinear Element	48
2.2.4	Dynamic (Small-Signal) Resistance of a Nonlinear Element	49
2.2.5	Electronic Switch	50
2.3	Independent Sources	52
2.3.1	Independent Ideal Voltage Source	52
2.3.2	Circuit Model of a Practical Voltage Source	54
2.3.3	Independent Ideal Current Source	55
2.3.4	Circuit Model of a Practical Current Source	57
2.3.5	Operation of the Voltage Source	58
2.3.6	Application Example: DC Voltage Generator with Permanent Magnets	59
2.3.7	Application Example: Chemical Battery	61
2.4	Dependent Sources and Time-Varying Sources	64
2.4.1	Dependent Versus Independent Sources	64
2.4.2	Definition of Dependent Sources	64
2.4.3	Transfer Characteristics	66
2.4.4	Time-Varying Sources	67
2.5	Ideal Voltmeter and Ammeter: Circuit Ground	69
2.5.1	Ideal Voltmeter and Ammeter	69
2.5.2	Circuit Ground: Fluid Mechanics Analogy	70
2.5.3	Types of Electric Ground	71
2.5.4	Ground and Return Current	71
2.5.5	Absolute Voltage and Voltage Drop Across a Circuit Element	72
3	Circuit Laws and Networking Theorems	89
3.1	Circuit Laws: Networking Theorems	91
3.1.1	Electric Network and Its Topology	91
3.1.2	Kirchhoff's Current Law	93
3.1.3	Kirchhoff's Voltage Law	95
3.1.4	Power-Related Networking Theorems	98
3.1.5	Port of a Network: Network Equivalence	99
3.2	Series and Parallel Network/Circuit Blocks	100
3.2.1	Sources in Series and in Parallel	100
3.2.2	Resistances in Series and in Parallel	102
3.2.3	Reduction of Resistive Networks	104
3.2.4	Voltage Divider Circuit	105
3.2.5	Application Example: Voltage Divider as a Sensor Circuit	107

- 3.2.6 Application Example: Voltage Divider as an Actuator Circuit 109
- 3.2.7 Current Limiter 111
- 3.2.8 Current Divider Circuit 112
- 3.2.9 Wheatstone Bridge 113
- 3.3 Superposition Theorem and Its Use 116
 - 3.3.1 Linear and Nonlinear Circuits 116
 - 3.3.2 Superposition Theorem or Superposition Principle 117
 - 3.3.3 Y (Wye) and Δ (Delta) Networks: Use of Superposition 119
 - 3.3.4 T and Π Networks: Two-Port Networks 121
 - 3.3.5 General Character of Superposition Theorem 122
- 4 Circuit Analysis and Power Transfer 139**
 - 4.1 Nodal/Mesh Analysis 141
 - 4.1.1 Importance of Circuit Simulators 141
 - 4.1.2 Nodal Analysis for Linear Circuits 141
 - 4.1.3 Supernode 145
 - 4.1.4 Mesh Analysis for Linear Circuits 146
 - 4.1.5 Supermesh 147
 - 4.2 Generator Theorems 149
 - 4.2.1 Equivalence of Active One-Port Networks: Method of Short/Open Circuit 149
 - 4.2.2 Application Example: Reading and Using Data for Solar Panels 150
 - 4.2.3 Source Transformation Theorem 151
 - 4.2.4 Thévenin's and Norton's Theorems: Proof Without Dependent Sources 153
 - 4.2.5 Application Example: Generating Negative Equivalent Resistance 158
 - 4.2.6 Summary of Circuit Analysis Methods 159
 - 4.3 Power Transfer 160
 - 4.3.1 Maximum Power Transfer 160
 - 4.3.2 Maximum Power Efficiency 162
 - 4.3.3 Application Example: Power Radiated by a Transmitting Antenna 163
 - 4.3.4 Application Example: Maximum Power Extraction from Solar Panel 164
 - 4.4 Analysis of Nonlinear Circuits: Generic Solar Cell 167
 - 4.4.1 Analysis of Nonlinear Circuits: Load Line Method 167
 - 4.4.2 Iterative Method for Nonlinear Circuits 169
 - 4.4.3 Application Example: Solving the Circuit for a Generic Solar Cell 170

Contents

- 5 Operational Amplifier and Amplifier Models 189**
 - 5.1 Amplifier Operation and Circuit Models 191
 - 5.1.1 Amplifier Operation 191
 - 5.1.2 Application Example: Operational Amplifier Comparator 194
 - 5.1.3 Amplifier Circuit Model 195
 - 5.1.4 Ideal-Amplifier Model and First Summing-Point Constraint 197
 - 5.2 Negative Feedback 199
 - 5.2.1 Idea of the Negative Feedback 199
 - 5.2.2 Amplifier Feedback Loop: Second Summing-Point Constraint 199
 - 5.2.3 Amplifier Circuit Analysis Using Two Summing-Point Constraints 201
 - 5.2.4 Mathematics Behind the Second Summing-Point Constraint 205
 - 5.2.5 Current Flow in the Amplifier Circuit 206
 - 5.2.6 Multiple-Input Amplifier Circuit: Summing Amplifier 207
 - 5.3 Amplifier Circuit Design 209
 - 5.3.1 Choosing Proper Resistance Values 209
 - 5.3.2 Model of a Whole Voltage Amplifier Circuit 211
 - 5.3.3 Voltage Amplifier Versus Matched Amplifier 212
 - 5.3.4 Cascading Amplifier Stages 215
 - 5.3.5 Amplifier DC Imperfections and Their Cancellation 217
 - 5.3.6 DC-Coupled Single-Supply Amplifier: Virtual-Ground Circuit 220
 - 5.4 Difference and Instrumentation Amplifiers 222
 - 5.4.1 Differential Input Signal to an Amplifier 222
 - 5.4.2 Difference Amplifier: Differential Gain and Common-Mode Gain 223
 - 5.4.3 Application Example: Instrumentation Amplifier 225
 - 5.4.4 Instrumentation Amplifier in Laboratory 228
 - 5.5 General Feedback Systems 230
 - 5.5.1 Signal-Flow Diagram of a Feedback System 230
 - 5.5.2 Closed-Loop Gain and Error Signal 230
 - 5.5.3 Application of General Theory to Voltage Amplifiers with Negative Feedback 232
 - 5.5.4 Voltage, Current, Transresistance, and Transconductance Amplifiers with the Negative Feedback 233

Part II Transient Circuits

6	Dynamic Circuit Elements	259
6.1	Static Capacitance and Inductance	261
6.1.1	Capacitance, Self-Capacitance, and Capacitance to Ground	261
6.1.2	Application Example: ESD	263
6.1.3	Parallel-Plate Capacitor	264
6.1.4	Circuit Symbol: Capacitances in Parallel and in Series	266
6.1.5	Application Example: How to Design a 1- μ F Capacitor?	267
6.1.6	Application Example: Capacitive Touchscreens	270
6.1.7	Self-Inductance (Inductance) and Mutual Inductance	272
6.1.8	Inductance of a Solenoid With and Without Magnetic Core	273
6.1.9	Circuit Symbol: Inductances in Series and in Parallel	275
6.1.10	Application Example: How to Design a 1-mH Inductor?	276
6.2	Dynamic Behavior of Capacitance and Inductance	278
6.2.1	Set of Passive Linear Circuit Elements	278
6.2.2	Dynamic Behavior of Capacitance	278
6.2.3	Dynamic Behavior of Inductance	281
6.2.4	Instantaneous Energy and Power of Dynamic Circuit Elements	283
6.2.5	DC Steady State	284
6.2.6	Behavior at Very High Frequencies	285
6.3	Application Circuits Highlighting Dynamic Behavior	287
6.3.1	Bypass Capacitor	287
6.3.2	Blocking Capacitor	289
6.3.3	Decoupling Inductor	289
6.3.4	Amplifier Circuits With Dynamic Elements: Miller Integrator	290
6.3.5	Compensated Miller Integrator	291
6.3.6	Differentiator and Other Circuits	292
7	Transient Circuit Fundamentals	307
7.1	RC Circuits	310
7.1.1	Energy-Release Capacitor Circuit	310
7.1.2	Time Constant of the RC Circuit and Its Meaning	312
7.1.3	Continuity of the Capacitor Voltage	313
7.1.4	Application Example: Electromagnetic Railgun	314

Contents

7.1.5	Application Example: Electromagnetic Material Processing	316
7.1.6	Application Example: Digital Memory Cell	317
7.1.7	Energy-Accumulating Capacitor Circuit	318
7.2	RL Circuits	321
7.2.1	Energy-Release Inductor Circuit	321
7.2.2	Continuity of the Inductor Current	324
7.2.3	Energy-Accumulating Inductor Circuit	325
7.2.4	Energy-Release RL Circuit with the Voltage Supply	327
7.2.5	Application Example: Laboratory Ignition Circuit	328
7.3	Switching RC Oscillator	330
7.3.1	About Electronic Oscillators	330
7.3.2	Bistable Amplifier Circuit with the Positive Feedback	330
7.3.3	Triggering	332
7.3.4	Switching RC Oscillator	333
7.3.5	Oscillation Frequency	334
7.3.6	Circuit Implementation: 555 Timer	335
7.4	Single-Time-Constant (STC) Transient Circuits	337
7.4.1	Circuits with Resistances and Capacitances	337
7.4.2	Circuits with Resistances and Inductances	339
7.4.3	Example of a Non-STC Transient Circuit	341
7.4.4	Example of an STC Transient Circuit	342
7.4.5	Method of Thévenin Equivalent and Application Example: Circuit with a Bypass Capacitor	343
7.5	Description of the Second-Order Transient Circuits	346
7.5.1	Types of Second-Order Transient Circuits	346
7.5.2	Series-Connected Second-Order RLC Circuit	346
7.5.3	Initial Conditions in Terms of Circuit Current and Capacitor Voltage	349
7.5.4	Step Response and Choice of the Independent Function	350
7.5.5	Parallel Connected Second-Order RLC Circuit	351
7.6	Step Response of the Series RLC Circuit	354
7.6.1	General Solution of the Second-order ODE	354
7.6.2	Derivation of the Complementary Solution: Method of Characteristic Equation	354
7.6.3	Finding Integration Constants	356
7.6.4	Solution Behavior for Different Damping Ratios	356
7.6.5	Overshoot and Rise Time	357
7.6.6	Application Example: Nonideal Digital Waveform	358

Part III AC Circuits

8	Steady-State AC Circuit Fundamentals	389
8.1	Harmonic Voltage and Current: Phasor	391
8.1.1	Harmonic Voltages and Currents	391
8.1.2	Phase: Leading and Lagging	393
8.1.3	Application Example: Measurements of Amplitude, Frequency, and Phase	396
8.1.4	Definition of a Phasor	396
8.1.5	From Real Signals to Phasors	398
8.1.6	From Phasors to Real Signals	399
8.1.7	Polar and Rectangular Forms: Phasor Magnitude	399
8.1.8	Operations with Phasors and Phasor Diagram	401
8.1.9	Shorthand Notation for the Complex Exponent	404
8.2	Impedance	405
8.2.1	The Concept of Impedance	405
8.2.2	Physical Meaning of Impedance	407
8.2.3	Magnitude and Phase of Complex Impedance	408
8.2.4	Application Example: Impedance of a Human Body	410
8.3	Principles of AC Circuit Analysis	411
8.3.1	AC Circuit Analysis: KVL, KCL, and Equivalent Impedances	411
8.3.2	Complete Solution for an AC Circuit: KVL and KCL on Phasor Diagram	412
8.3.3	Source Transformation	413
8.3.4	Thévenin and Norton Equivalent Circuits	415
8.3.5	Summary of AC Circuit Analysis at a Single Frequency	417
8.3.6	Multifrequency AC Circuit Analysis: Superposition Theorem	417
9	Filter Circuits: Frequency Response, Bode Plots, and Fourier Transform	433
9.1	First-Order Filter Circuits and Their Combinations	435
9.1.1	RC Voltage Divider as an Analog Filter	435
9.1.2	Half-Power Frequency and Amplitude Transfer Function	440
9.1.3	Bode Plot, Decibel, and Roll-Off	441
9.1.4	Phase Transfer Function and Its Bode Plot	444
9.1.5	Complex Transfer Function: Cascading Filter Circuits	445
9.1.6	RL Filter Circuits	448
9.2	Bandwidth of an Operational Amplifier	451
9.2.1	Bode Plot of the Open-Loop Amplifier Gain	451

Contents

9.2.2	Unity-Gain Bandwidth Versus Gain-Bandwidth Product	452
9.2.3	Model of the Open-Loop AC Gain	453
9.2.4	Model of the Closed-Loop AC Gain	454
9.2.5	Application Example: Finding Bandwidth of an Amplifier Circuit	455
9.2.6	Application Example: Selection of an Amplifier IC for Proper Frequency Bandwidth	456
9.3	Introduction to Continuous and Discrete Fourier Transform	458
9.3.1	Meaning and Definition of Fourier Transform	458
9.3.2	Mathematical Properties of Fourier Transform	460
9.3.3	Discrete Fourier Transform and Its Implementation	461
9.3.4	Sampling Theorem	463
9.3.5	Applications of Discrete Fourier Transform	464
9.3.6	Application Example: Numerical Differentiation via the FFT	464
9.3.7	Application Example: Filter Operation for an Input Pulse Signal	466
9.3.8	Application Example: Converting Computational Electromagnetic Solution from Frequency Domain to Time Domain	467
10	Second-Order RLC Circuits	481
10.1	Theory of Second-Order Resonant RLC Circuits	483
10.1.1	Self-Oscillating Ideal LC Circuit	483
10.1.2	Series Resonant Ideal LC Circuit	485
10.1.3	Series Resonant RLC Circuit: Resonance Condition	486
10.1.4	Quality Factor Q of the Series Resonant RLC Circuit	488
10.1.5	Bandwidth of the Series Resonant RLC Circuit	490
10.1.6	Parallel Resonant RLC Circuit: Duality	493
10.2	Construction of Second-Order RLC Filters	496
10.2.1	Second-Order Band-Pass RLC Filter	496
10.2.2	Second-Order Low-Pass RLC Filter	499
10.2.3	Second-Order High-Pass RLC Filter	500
10.2.4	Second-Order Band-Reject RLC Filter	502
10.2.5	Second-Order RLC Filters Derived from the Parallel RLC Circuit	504
10.3	RLC Circuits for Near-Field Communications and Proximity Sensors	506
10.3.1	Near-Field Wireless Link	506
10.3.2	Transmitter Circuit	507
10.3.3	Receiver Circuit	508

- 10.3.4 Application Example: Near-Field Wireless Link in Laboratory 510
- 10.3.5 Application Example: Proximity Sensors 511
- 11 AC Power and Power Distribution 523**
- 11.1 AC Power Types and Their Meaning 525
 - 11.1.1 Instantaneous AC Power 525
 - 11.1.2 Time-averaged AC Power 526
 - 11.1.3 Application Example: rms Voltages and AC Frequencies Around the World 528
 - 11.1.4 rms Voltages for Arbitrary Periodic AC Signals 529
 - 11.1.5 Average AC Power in Terms of Phasors: Power Angle 531
 - 11.1.6 Average Power for Resistor, Capacitor, and Inductor 532
 - 11.1.7 Average Power, Reactive Power, and Apparent Power 533
 - 11.1.8 Power Triangle 535
 - 11.1.9 Application Example: Wattmeter 538
- 11.2 Power Factor Correction: Maximum Power Efficiency and Maximum Power Transfer 539
 - 11.2.1 Power Factor Correction 539
 - 11.2.2 Application Example: Automatic Power Factor Correction System 542
 - 11.2.3 Principle of Maximum Power Efficiency for AC Circuits 542
 - 11.2.4 Principle of Maximum Power Transfer for AC Circuits 544
- 11.3 AC Power Distribution: Balanced Three-Phase Power Distribution System 546
 - 11.3.1 AC Power Distribution Systems 546
 - 11.3.2 Phase Voltages: Phase Sequence 547
 - 11.3.3 Wye (Y) Source and Load Configurations for Three-Phase Circuits 549
 - 11.3.4 Application: Examples of Three-Phase Source and the Load 550
 - 11.3.5 Solution for the Balanced Three-Phase Wye-Wye Circuit 551
 - 11.3.6 Removing the Neutral Wire in Long-Distance Power Transmission 553
- 11.4 Power in Balanced Three-Phase Systems:
 - Delta-connected Three-Phase Circuits 556
 - 11.4.1 Instantaneous Power 556
 - 11.4.2 Average Power, Reactive Power, and Apparent Power 558

Contents

11.4.3	Application Example: Material Consumption in Three-Phase Systems	558
11.4.4	Balanced Delta-Connected Load	560
11.4.5	Balanced Delta-Connected Source	560
12	Electric Transformer and Coupled Inductors	577
12.1	Ideal Transformer as a Linear Passive Circuit Element . . .	579
12.1.1	Electric Transformer	579
12.1.2	Ideal Open-Circuited Transformer: Faraday's Law of Induction	579
12.1.3	Appearance of Transformer Currents	583
12.1.4	Ampere's Law	583
12.1.5	Ideal Loaded Transformer	584
12.1.6	Ideal Transformer Versus Real Transformer: Transformer Terminology	586
12.1.7	Mechanical Analogies of a Transformer	589
12.2	Analysis of Ideal Transformer Circuits	590
12.2.1	Circuit with a Transformer in the Phasor Form	590
12.2.2	Referred (Or Reflected) Source Network in the Secondary Side	590
12.2.3	Referred (Or Reflected) Load Impedance to the Primary Side	592
12.2.4	Transformer as a Matching Circuit	593
12.2.5	Application Example: Electric Power Transfer via Transformers	595
12.3	Some Useful Transformers	598
12.3.1	Autotransformer	598
12.3.2	Multiwinding Transformer	599
12.3.3	Center-Tapped Transformer: Single-Ended to Differential Transformation	600
12.3.4	Current Transformer	602
12.4	Real-Transformer Model	604
12.4.1	Model of a Nonideal Low-Frequency Transformer	604
12.4.2	Model Parameters and Their Extraction	604
12.4.3	Analysis of Nonideal Transformer Model	606
12.4.4	Voltage Regulation and Transformer Efficiency	609
12.4.5	About High-Frequency Transformer Model	610
12.5	Model of Coupled Inductors	612
12.5.1	Model of Two Coupled Inductors	612
12.5.2	Analysis of Circuits with Coupled Inductors	613
12.5.3	Coupling Coefficient	616
12.5.4	Application Example: Wireless Inductive Power Transfer	618
12.5.5	Application Example: Coupling of Nearby Magnetic Radiators	622

Part IV Digital Circuits

- 13 Switching Circuits** 641
 - 13.1 Principle of Operation 643
 - 13.1.1 Switch Concept 643
 - 13.1.2 Switch Position in a Circuit 644
 - 13.1.3 MOSFET Switches and Threshold Voltage 645
 - 13.1.4 Sketch of Transistor Physics 647
 - 13.2 Power Switching Circuits 650
 - 13.2.1 Switching Quadrants 650
 - 13.2.2 Switching a Resistive Load 651
 - 13.2.3 Switching a DC Motor 651
 - 13.2.4 One-Quadrant Switch for a DC Motor 652
 - 13.2.5 Half H-Bridge for a DC Motor 653
 - 13.2.6 Full H-Bridge for a DC Motor 655
 - 13.2.7 Application Example: Pulse-Width Modulation (PWM) Motor Controller
PWM Voltage Form 657
 - 13.3 Digital Switching Circuits 660
 - 13.3.1 NOT Gate or Logic Inverter 660
 - 13.3.2 NOR Gate and OR Gate 661
 - 13.3.3 NAND Gate and AND Gate 664
 - 13.3.4 Simple Combinational Logic Circuits:
Switching Algebra 668
 - 13.3.5 Universal Property of NAND Gates:
De Morgan’s Laws 669
 - 13.3.6 Logic Circuit Analysis and Application
Example: Logic Gate Motor Controller 670
 - 13.3.7 Logic Circuit Synthesis 672
 - 13.3.8 The Latch 673
- 14 Analog-to-Digital Conversion** 689
 - 14.1 Digital Voltage and Binary Numbers 691
 - 14.1.1 Introduction: ADC and DAC Circuits 691
 - 14.1.2 Analog Voltage Versus Digital Voltage 692
 - 14.1.3 Bit Rate, Clock Frequency: Timing Diagram 695
 - 14.1.4 Binary Numbers 698
 - 14.1.5 Hexadecimal Numbers 700
 - 14.1.6 ASCII Codes and Binary Words 702
 - 14.1.7 Tri-state Digital Voltage 704
 - 14.2 Digital-to-Analog Converter 707
 - 14.2.1 Digital-to-Analog Converter 707
 - 14.2.2 Circuit (A Binary-Weighted-Input DAC) 707
 - 14.2.3 Underlying Math and Resolution Voltage 708
 - 14.2.4 DAC Full-Scale Output Voltage Range,
Resolution, and Accuracy 711
 - 14.2.5 Other DAC Circuits 714

Contents

14.3	Sample-and-Hold Circuit: Nyquist Rate	717
14.3.1	Analog-to-Digital Converter	717
14.3.2	A Quick Look at an Analog Sinusoidal Voltage	717
14.3.3	Sample-and-Hold Voltage	719
14.3.4	Sample-and-Hold Circuit (SH Circuit)	720
14.3.5	Nyquist Rate	721
14.4	Analog-to-Digital Converter	724
14.4.1	Flash ADC	724
14.4.2	ADC Resolution in Bits, Full-Scale Input Voltage Range, and Voltage Resolution . . .	726
14.4.3	ADC Equation and Quantization Error	726
14.4.4	Successive-Approximation ADC	728
15	Embedded Computing	745
15.1	Architecture of Microcontrollers	747
15.1.1	A Generic Microcontroller	747
15.1.2	Central Processing Unit	748
15.1.3	Memory	749
15.1.4	Input and Output Devices	750
15.1.5	Timers	750
15.1.6	Buses	750
15.1.7	Universal Synchronous/Asynchronous Receiver/Transmitter (USART)	751
15.2	Memory	753
15.2.1	Organization of Memory	753
15.2.2	Types of Memory	755
15.2.3	Flash Memory in Embedded Devices	756
15.3	Arduino Uno: An Embedded Microcontroller	757
15.3.1	What Is Arduino?	757
15.3.2	Arduino IDE	757
15.3.3	Getting Started with Arduino IDE	758
15.3.4	Arduino Language, Program Storage, and Basic Program Setup	759
15.3.5	Compiling and Uploading Code to Arduino Uno	761
15.4	Basic Arduino Syntax	762
15.4.1	Data Types	762
15.4.2	Assignment Statements and Their Features	763
15.4.3	Arithmetic Operations	764
15.4.4	Functions	765
15.4.5	Libraries	767
15.4.6	Objects. Application Example: A Servomotor . . .	768
15.4.7	Interfacing with IO Pins	769
15.5	More Advanced Arduino Programming	771
15.5.1	Conditional Statements	771
15.5.2	Switch Statements	773

15.5.3 Loops 774
15.5.4 Arrays and Strings 777
15.5.5 Serial Communication 779
15.5.6 Interrupts. Application Example:
Emergency Motor Stop 780
15.5.7 Square Wave and PWM Generation
with Arduino 782

Part V Diode and Transistor Circuits

16 Electronic Diode and Diode Circuits 795
16.1 Diode Operation and Classification 797
16.1.1 Circuit Symbol and Terminals 797
16.1.2 Three Regions of Operation 797
16.1.3 Mechanical Analogy of Diode Operation 798
16.1.4 Forward-Bias Region: Switching Diode 798
16.1.5 Reverse-Bias Region: Varactor Diode 800
16.1.6 Breakdown Region: Zener Diode 801
16.1.7 Other Common Diode Types 801
16.2 Diode Models 804
16.2.1 Ideal-Diode Model: Method of Assumed
States 804
16.2.2 Constant-Voltage-Drop Model 808
16.2.3 Exponential Model in the Forward-Bias
Region and Its Use 809
16.2.4 Load-Line Analysis 810
16.2.5 Iterative Solution 811
16.2.6 Linearization About a Bias Point:
Small-Signal Diode Model 811
16.2.7 Superposition Principle for Small-Signal
Diode Model 813
16.3 Diode Voltage Regulators and Rectifiers 814
16.3.1 Voltage Reference and Voltage Regulator 814
16.3.2 Voltage Regulator with Zener Diode 815
16.3.3 Half-Wave Rectifier 817
16.3.4 Full-Wave Rectifier with a Dual Supply 819
16.3.5 Diode Bridge Rectifier 820
16.3.6 Application Example: Automotive
Battery-Charging System 821
16.3.7 Application Example: Envelope (or Peak)
Detector Circuit 823
16.4 Diode Wave-Shaping Circuits 827
16.4.1 Diode Clamper Circuit (DC Restorer) 827
16.4.2 Diode Voltage Doubler and Multiplier 828
16.4.3 Positive, Negative, and Double Clipper 830
16.4.4 Transfer Characteristic of a Diode Circuit 832

Contents

17	Bipolar Junction Transistor and BJT Circuits	851
17.1	Physical Principles and Operation Laws	853
17.1.1	Physical Structure: Terminal Voltages and Currents	853
17.1.2	Principle of Operation	854
17.1.3	Operating Regions	856
17.1.4	Active Region	857
17.1.5	Saturation Region and Cutoff Region	859
17.1.6	Transistor v - i Dependencies	861
17.1.7	Early Effect	863
17.1.8	The pnp Transistor	863
17.2	Large-Signal Circuit Models of a BJT	866
17.2.1	Large-Signal Circuit Model of a BJT	866
17.2.2	Large-Signal DC Circuit Model of a BJT	868
17.2.3	Method of Assumed States	870
17.2.4	Transistor Circuit Analysis Using the Method of Assumed States	871
17.2.5	DC Transistor Bias Circuits	873
17.2.6	β -Independent Biasing and Negative Feedback	874
17.2.7	Common Discrete-Circuit Bias Arrangement	876
17.2.8	Other Bias Circuits	878
17.3	Practical BJT Circuits at DC	880
17.3.1	Constant-Current Sources: Active Region of Operation	880
17.3.2	Voltage Follower (Voltage Buffer): Active Region of Operation	882
17.3.3	BJT Switches: Saturation Region	884
17.3.4	Application Example: Automotive BJT Dome Light Switch	886
17.3.5	Application Example: Door Lock BJT Switch and Darlington Pair	887
17.4	Small-Signal Transistor Amplifier	889
17.4.1	Generic Voltage-Gain Amplifier	889
17.4.2	Simplified Model of the BJT Common-Emitter Amplifier	890
17.4.3	Small-Signal BJT Analysis and Superposition	892
17.4.4	Analysis of Small-Signal Common-Emitter Amplifiers	894
17.4.5	Application Example: Transistor Amplifier Bandwidth	898
18	MOS Field-Effect Transistor (MOSFET)	919
18.1	Principle of Operation and Threshold Voltage	921
18.1.1	Physical Structure: Terminal Voltages and Currents	921
18.1.2	Simplified Principle of Operation	923
18.1.3	NMOS Capacitor	924

Contents

18.1.4	Voltage Across the Oxide Layer Before and at the Onset of Strong Inversion	925
18.1.5	Voltage Across the Semiconductor Body	926
18.1.6	Threshold Voltage	928
18.1.7	PMOS Transistor	929
18.1.8	Oxide Thicknesses and Capacitances in CMOS Processes	930
18.1.9	Family Tree of FETs	931
18.2	Theoretical Model of a MOSFET	932
18.2.1	Test Circuit and Operating Regions	932
18.2.2	Linear Subregion of Triode Region at Strong Inversion	933
18.2.3	Nonlinear Subregion of Triode Region at Strong Inversion	934
18.2.4	Saturation Region	935
18.2.5	The v-i Dependencies	937
18.2.6	PMOS Transistor	939
18.2.7	Large-Signal MOSFET Model in Saturation	939
18.2.8	Device Parameters in CMOS Processes	940
18.3	MOSFET Switching and Bias Circuits	942
18.3.1	Triode Region for Switching Circuits: Device Parameter Extraction	942
18.3.2	Resistor-Switch Model in Triode Region	944
18.3.3	Application Example: Output Resistance of Digital Logic Gates	945
18.3.4	MOSFET Circuit Analysis at DC	947
18.3.5	Application Example: Basic MOSFET Actuator	951
18.4	MOSFET Amplifier	953
18.4.1	MOSFET Common-Source Amplifier	953
18.4.2	Voltage Transfer Characteristic	953
18.4.3	Principle of Operation and Q-Point	955
18.4.4	MOSFET Biasing for Amplifier Operation	956
18.4.5	Small-Signal MOSFET Model and Superposition	956
18.4.6	MOSFET Transconductance	957
18.4.7	Analysis of Common-Source MOSFET Amplifier	958
	Erratum	E1
	Index	973