

# Index

## A

- abc* phase sequence, 547, 573
- Absolute voltages in circuit, 72–73
- acb* phase sequence, 548, 554, 573
- AC circuit analysis
  - KVL, KCL and equivalent impedances, 411–412
  - Norton equivalent circuits, 415–417
  - phasor diagram, 412–413
  - single frequency, 417
  - source transformation, 413–415
  - superposition theorem, 417–418
  - Thévenin equivalent circuits, 415–417
- AC-coupled amplifier, 208
- AC-direct micro-hydropower system, 79
- AC fuse, 528, 529
- AC power
  - distribution system
    - automotive alternator, 550
    - line currents, 553–554
    - line voltages, 551–553
    - neutral conductor, 546
    - polyphase distribution systems, 546
    - phase voltages, 551–553
    - residential household, 551
    - single-phase three-wire, 546
    - single-phase two-wire, 546, 547
    - synchronous three-phase AC generator, 550
    - synchronous three-phase AC motor, 550–551
    - three-phase four-wire, 546
  - electronic circuits, 525
  - load voltage amplitude, 525
  - maximum power efficiency, 542–543, 571, 572
  - maximum power transfer
    - average power, 544
    - equality, 544
    - impedance matching, 545
    - load impedance, 545
    - radio-frequency and communication circuits, 544
  - Ohm's law, 525
  - rms voltage
    - and AC frequencies, 528–529
    - and rms current, 526–528
    - time averaging, 526, 567
- Active differentiator, 292
- Active filters, 290
- Active one-port networks, 178
- Active reference configuration, 52
- AC voltage source, 68
- Air-core coil, 275
- Alternating-current (AC)
  - circuits (*see* AC circuit analysis)
  - power (*See* AC power)
- American Wire Gauge (AWG), 39, 78
- Ampere's law, 583–584, 631
- Amplifier
  - circuit analysis (*see* Amplifier circuit analysis)
  - circuit model, 195–197
  - differential gain and common-mode gain, 223–225
  - differential input signal, 222–223
  - dynamic circuit elements, 283–284, 290–291
  - ideal-amplifier model, 197–198
  - input/output resistances, 198
  - instrumentation, 226–229
  - load cell and uses, 229
  - output current, 198
  - summing-point constraint, 197–198
- Amplifier circuit analysis
  - cascading amplifier stages, 215–217
  - current flow, 206–207
  - DC imperfections, 217–220
  - discrete resistance values, 210
  - gain tolerance, 210–211
  - input bias and offset currents, 219–220
  - input load bridging, 212–214
  - input load matching, 214–215
  - input offset voltage, 217–218
  - input/output resistances, 211–212
  - inverting amplifier, 203–204

---

The original version of the index was revised. An erratum can be found at DOI [10.1007/978-3-319-21173-2\\_19](https://doi.org/10.1007/978-3-319-21173-2_19)

- Amplifier circuit analysis (*cont.*)
    - multiple-input, 207–208
    - negative feedback, 211
    - non-inverting amplifier, 201–203
    - output offset voltage, 218–219
    - potentiometers, 210
    - resistance values, 209–210
    - summing-point constraints, 240
    - voltage follower/buffer amplifier, 204–205
    - voltage vs. matched amplifier, 212–215
  - Amplitude envelope, 824
  - Amplitude-modulated signal, 479
  - Amplitude transfer function *See* Filter circuits
  - Analog computers, 293, 698–699
  - Analog filter
    - amplitudes, 436
    - DC circuit, 436
    - load connection, effect, 439–440
    - qualitative analysis, 436–437
    - RC voltage divider circuit, 435, 436, 473
    - real-valued voltages, 436
    - transient circuits, 436
    - two-port network, 437–439
  - Analog output voltage, 692
  - Analog pulse counter, 290
  - Analog sinusoidal voltage, 717–718
  - Analog to digital converter (ADC)
    - conversion time, 727–728
    - and DAC circuit, 691–692
    - equation, 726–727
    - flash, 724–725
    - quantization error, 727
    - speed and throughput rate, 727–728
    - successive-approximation
      - circuit, 728
      - concept, 728
      - DAC formula, 730
      - logic control block, 729
      - operation, 730
  - AND gate, 664–667
  - Apparent power, 535
  - Arbitrary linear networks, 155–157
  - Arduino
    - applications, 757
    - compiling and uploading code, 761
    - IDE, 757–759
    - language and compiler, 759
    - loop() function, 760
    - open-source platform, 757
    - setup() function, 760
    - sketch, 760
    - translation, 761
  - Arduino programming
    - arrays, 777–779
    - conditional statements, 771–773
    - interrupts, 780–782
    - loops, 774–777
    - PWM generation, 782–783
    - serial communication, 779–780
    - square wave generation, 782–783
    - strings, 777–779
    - switch statements, 773–774
  - Arduino syntax
    - arithmetic operations, 764–765
    - assignment statements and features, 763–764
    - data types, 762
    - functions, 769
    - interfacing, IO pins, 769–770
    - library, 767
    - objects, 768–769
  - Arithmetic operations
    - characters and relation, C language, 765
    - floating point and integer, 764
    - IDE, 765
    - typecasting, 764
  - Arrays
    - element, 777
    - indexing, 777
    - linear, 777
  - ASCII codes, 702–704, 735
  - Assignment statements
    - declaration, 763
    - floating points, 763
    - MOTOR\_PIN, 763
    - typecasting, 764
  - Astable multivibrator, 330
  - Asynchronous transmission, 698
  - Autotransformer, 598–599, 635
  - Average generator voltage, 60
  - Average power, 532–533, 569
- B**
- Balanced delta-connected load, 560, 575
  - Balanced delta-connected source, 560–563, 575
  - Balanced phase voltages, 578, 552
  - Balanced three-phase load, 549
  - Balanced three-phase source, 549
  - Balanced three-phase systems
    - apparent power, 556, 558
    - average power, 556, 558
    - constant torque, 557
    - line currents, 557
    - material consumption, 558–560
    - phase voltages, 557
    - reactive power, 556, 558
    - total instantaneous load power, 556
    - wye-wye configuration, 556
  - Balanced Y and  $\Delta$  networks, 121
  - Bandlimited spectrum, 459, 461, 463
  - Bandwidth, parallel resonant circuit, 495
  - Base-emitter voltage, 854, 855, 861, 867, 871, 872, 892
  - Battery capacity, 61, 62
  - Battery energy storage, 63
  - Battery pack, 100
  - Battery voltage, 61

- Bias circuit, dual-polarity power supply, 878
  - Bidirectional switch, 50
  - Binary counter, 208, 709
  - Binary numbers
    - analog computers, 699
    - ASCII codes, 702–704
    - conversion, 698–700
    - decimal fraction, 700
    - digital voltage, 692–693
    - MATLAB, 700
  - Binary-weighted-input DAC, 707–708
  - Bipolar junction transistor (BJT), 20
    - assumed states, 870
    - automotive dome light application, 886–887
    - base-collector (bias) voltage, 853
    - base-collector voltage, 854, 861
    - base current, 853
    - base-emitter (bias) voltage, 853
    - bias circuits, 878–879
    - collector current, 853
      - base current, 858–859
      - qualitative description, 857
      - Shockley equation, 857–858
    - collector-emitter (bias) voltage, 853
    - constant-current sources
      - circuit limitations, 881
      - collector current, 880, 881
      - color LEDs, 881, 882
      - fixed resistance, 880
      - LED driver, 881–882
    - DC transistor bias circuits, 873–874
    - dome light switch, 886–887
    - door lock BJT switch and Darlington pair, 887–888
    - early effect, 863
    - early voltage, 863, 907
    - EBJ and CBJ, 853
    - emitter current, 853
    - ground-side switches, 884
    - independent biasing and negative feedback, 874–875
    - large-signal DC circuit model, 868–870
    - maximum load current, 886
    - negative-side and positive-side, 884
    - npn BJT switch, 884–885
    - npn-junction transistor, 853, 854
      - operating regions, 856
    - overdriving, transistor base, 886
    - pnp transistor, 863–865
    - principles
      - built-in electric potential, 855
      - common-emitter configuration, 854
      - doping profiles, 854, 855
      - electron-controlling device, 856
      - intrinsic Fermi energy level of electrons, 855
      - potential boundary, 855
    - qualitative description
      - base current, 859, 860
      - collector current, 859, 860
      - diffusion electron motion, 859
      - Ebers-Moll model, 860
      - emitter current, 859, 860
      - forced common-emitter current gain, 860
      - forward-biased pn-junctions, 859
      - reverse common-emitter current gain, 860
    - transistor  $v$ - $i$  dependencies, 861–863
    - voltage-controlled switches, 884
    - voltage follower
      - circuit comparison, 882, 883
      - circuit limitations, 883–884
      - constant-voltage, 882
      - emitter follower configuration, 882
      - Thévenin equivalents, 883
  - Bistable amplifier circuit *See* Switching RC oscillator
  - Bit rate, 695–696
  - Blocking capacitor, 289
  - Body capacitance, 263
  - Body control module, 886
  - Boolean algebra, 668, 669, 670
  - Boolean expressions, 669, 673, 686
  - Branch currents, 93
  - Branch voltages, 93
  - Branches of electric network, 91–93
  - Break frequency
    - amplifier gain, 452
    - 3-dB frequency, 443
    - half-power frequency, 440
    - high-pass filter, 440–441, 447
    - mirror reflected, 444
  - Built-in voltage, pn-junction, 797, 799
  - Butterworth response, 499–501
  - Bypass capacitor, 287–288
- ## C
- Capacitance
    - conductors, 261
    - dynamic behavior, 278–286
    - equal conductors separated, large distances, 262
    - ground, 261–262
  - Capacitive coupling of an amplifier, 209
  - Capacitive reactance, 534
  - Capacitive touch screens, 265
  - Cascading amplifier stages, 215–217
  - Center-tapped transformer
    - 180° power divider, 602
    - 180° power splitter, 602
  - Central processing unit (CPU)
    - brain, 748
    - functions, 748
    - instruction, 748
    - instruction set, 748, 749
    - opcode, 748
    - operands, 748
    - software, 749
  - Channel pinch-off, 936
  - Charge separation principle, 58
  - Chassis ground, 71, 72
  - Circuit analysis methods, 159–163, 183
  - Circuit components

- Circuit components (*cont.*)
  - bias, 46
  - vs. circuit elements, 31
  - semiconductor, 20
- Circuit elements
  - absolute voltage and voltage drop, 72–73
  - vs. circuit components, 31
  - current amplifier, 65
  - ideal-diode, 49
  - independent ideal voltage source, 52
  - linear passive, 33
  - nonlinear passive, 47–48
  - transconductance amplifier, 65
  - transresistance amplifier, 66
  - $v$ - $i$  characteristic, 34–35
- Clamp on ammeter, 602
- Clock frequency, 696, 698
- Closed-loop AC gain, 453–455
- Closed-loop configuration, 192, 231
- Closed-loop gain, 202, 230–232
- CMOS NAND gate, 946–947
- CMOS NOT gate (inverter), 945
- Collector-base junction (CBJ), 853, 856
- Collector-emitter voltage, 854, 855, 861, 862, 867, 871, 873
- Common-base configuration, 854
- Common-base current gain, 858, 862, 906
- Common-collector configuration, 854
- Common-emitter amplifier
  - fixed-base transistor bias circuit, 890
  - linear expansion, 890–891
  - small-signal ground, 891
  - small-signal resistance/impedance, 890
  - voltage transfer characteristic, 890
- Common ground, dual-polarity power supply, 101
- Common-mode amplifier circuit gain, 224
- Common-mode input signal, 197
- Common-mode rejection ratio (CMRR), 224
- Common-mode voltage of sensor, 222, 224, 226
- Common (neutral) terminal (ground), 71
- Common-source MOSFET amplifier
  - DC bias solution, 958
  - input/output voltages, 959
  - large-signal/small-signal, 959
  - saturation region, 959
  - small-signal model, 959
  - voltage-controlled current source, 953
- Comparator, 194–195
- Compensated Miller integrator, 291–292
- Complementary MOS (CMOS) circuits
  - H-bridge, 658
  - logic inverter/NOT gate, 660
  - NAND logic gate, 665
  - NOR logic gate, 662
- Complementary transistors, 646
- Complex load power, balanced three-phase system, 558
- Complex power, 535
- Complex transfer function
  - cascading filter circuits, 445–447, 476
  - complex expression, 445
  - frequency response, 445
  - high-pass filter, 445
  - low-pass filter, 445, 446
  - next-stage filter load, 447–448
- Compliance, 19
- Conditional statements
  - function, 772
  - logic circuit, 772
  - logical expression, 772
  - nested if statements, 773
  - state programming, 771
  - structure, 771
- Conductance
  - Ohm's law, 33
  - transconductance, 65
- Conduction angle, 819
- Conservative field, 5
- Constant-voltage-drop model
  - assumed states, 808
  - diode current, 809
  - diode voltage, 809
  - voltage supply, 808
- Contour integral, 5
- Control switching circuits
  - full H-bridge switch, 650
  - half H-bridge, 650
  - motor speed controller, 650
  - one-quadrant switch, 650
- Corner frequency, 443, 444
- Coulomb force, 3, 7, 37, 94
- Coupled inductors
  - mutual inductances, 615
  - N coupled, 615
  - phasor form, 613, 614
  - T-network, 615–616
  - two coupled inductors, 616, 638
- Coupling coefficient
  - energy, 616
  - ideal transformer, 616–617
  - mutual inductance, 617
- CPU *See* Central processing unit (CPU)
- Current amplifier
  - current-controlled current source, 65
  - and transconductance, 233
  - using op-amp, 209
- Current-controlled current source, 65
- Current-controlled voltage source, 65–66
- Current divider circuit, 112–113
- Current division rule, 112
- Current limiter, 111–112
- Current-limiting resistor, 111, 134
- Current reference directions, 587, 613
- Current transformer, 602
- Cutoff frequency, 496, 497

**D**

- DAC *See* Digital to analog converter (DAC)
- DAC scaling voltage factor, 708
- Damping coefficient, 348, 352, 353, 358, 381
- Data bus, 707
- Data storage methods, 755
- Data types, 762
- 3-dB frequency, 443
- DC-coupled amplifier, 208
- DC-coupled single-supply amplifier, 220–221
- DC imperfections, 217–220
- DC operating point, 810, 811, 842, 843
- DC restorer circuit, 827, 828
- DC steady state, 284–285
- Decoupling capacitor, 289
- Decoupling inductor, 289
- Decrement operator, 775
- Delta-delta distribution system, 561
- $\Delta$  to Y transformation, 120, 121
- De Morgan's laws, 669–670
- Dependent sources
  - vs. independent sources, 64
- Depletion-enhancement mode MOSFET, 921
- Depletion-mode MOSFET, 921
- Device under test (DUT), 264
- DFT *See* Discrete Fourier transform (DFT)
- Differential amplifier circuit gain, 224
- Differential input signal, 197, 222–223
- Differential input voltage, 192, 200, 224
- Differential resistance, 49
- Differential sensor, 223
- Differentiator amplifier
  - circuit, 292–293
  - gain at very high frequencies, 292
- Digital logic gates
  - CMOS NOT gate, 945
  - logic inverter, 945
  - output resistance, 945–947
- Digital memory element, 332
- Digital output voltage, 694
- Digital repeater, 194
- Digital signal processing (DSP), 464, 691, 707
- Digital switching circuits
  - AND gate, 665–667
  - combinational logic circuits, 668–669
  - latch, 673
  - logic circuit analysis
    - motor state, 671–672
    - truth table, 670–671
  - logic circuit synthesis, 672–673
  - logic gate, 660
  - NAND gate, 664–665
  - NOR gate, 661–663
  - NOT gate/logic inverter, 660–661
  - OR gate, 663–664
  - universal property, NAND gates, 669–670
- Digital to analog converter (DAC)
  - binary-weighted-input, 707–708
  - equation, 711
  - math voltage, 708–709
  - operations, 707
  - output voltage range, 711
  - PWM, 716
  - quantization levels, 711
  - R/2R ladder, 714–716
  - relative accuracy, 712–714,
  - resolution, 712
  - resolution voltage, 709–710
  - Thévenin equivalent, 715–716
- Digital voltage
  - ADC, 691–692
  - vs. analog voltage, 692
  - ASCII codes and binary words, 702
  - binary numbers, 692, 693, 698–700
  - bit rate, 695–696
  - clock frequency, 696–697
  - hexadecimal numbers, 700–702
  - parallel vs. serial representation, 693, 694
  - timing diagram, 697, 698
  - tri-state, 704–705
- Digital-to-analog converter (DAC), 207, 247
- Diode, 20
  - bridge rectifier, 820, 821
  - clamper circuit, 827–828, 847
  - electronic (*see* Electronic diode)
  - voltage
    - doubler, 847
    - multiplier, 847
    - quadrupler circuit, 829
- Discrete-circuit transistor amplifiers
  - base-emitter loop, 874
  - four-resistor bias circuit, 876
  - integrated-circuit transistor amplifiers, 876
  - Thévenin equivalent, 876, 877
  - voltage supply, 876
- Discrete Fourier transform (DFT)
  - applications, 464
  - definition, 462–463
  - FFT, 461
  - fundamental frequency, 461
  - IFFT, 461
  - implementation, 479–480
  - sampling interval, 461
  - sampling points, 461
  - spectrum, 463
- Dotted terminals, 582, 587, 600, 612, 635
- Double clipper, 831
- DRAM *See* Dynamic random-access memory (DRAM)
- DSP *See* Digital signal processing (DSP)
- Dual in-line (DIP-N) package, 191
- Dual-polarity power supply, 101
- Dynamic circuit elements
  - capacitance (*see* Capacitance)
  - instantaneous energy and power, 283–284
  - inductance (*see* Inductance)
- Dynamic random-access memory (DRAM), 317
- Dynamic resistance, 49

**E**

- Earth ground, 71, 72
- EAS *See* Electronic article surveillance (EAS)
- Electric circuit, 39, 53, 57, 69, 70, 71, 84
- Electric current density, 11
- Electric field intensity, 3
- Electric network
  - description, 92
  - topology, 92–95
- Electric permittivity, 9
- Electric transformer
  - AC power transfer, 579
  - Ampere's law, 583–584
  - application, 634–635
  - autotransformer, 598–599
  - center-tapped, 600–602, 636
  - current, 602–603, 636
  - fixed load voltage, 595–596
  - fixed source voltage, 596–597
  - function, 579, 580
  - high-frequency transformer model, 609–610
  - magnetic circuit, 579
  - mechanical analogies, 589
  - multiwinding, 599–600
  - phasor form, 590, 591, 633
  - referred load impedance, primary side, 592–593, 633
  - referred source network, secondary side, 590–592, 633
  - transformer currents, 583
  - transformer efficiency, 610, 637
  - usage, 579
  - voltage regulation, 609–610, 637
- Electromagnetic material processing
  - electromagnetic forming, 316–317
  - self-induced Lorentz force, 317
- Electronic article surveillance (EAS), 506
- Electronic diode
  - anode and cathode, 797
  - automotive battery-charging system
    - application, 845
    - delta/gye connection, 821
    - diode circuit transformation, 822
    - three-phase diode rectifier, 822–823
    - vehicle, 821
  - breakdown region, 797
  - constant-voltage-drop-diode model, 815, 830
  - diode clipper circuits, 830
  - diode limiter circuits, 830
  - double diode clipper circuit, 831
  - envelope/peak detector circuit
    - amplitude-modulated signal, 824
    - demodulation, 823
    - and operation, 824–826
    - square-law region, 826
  - ESD protection, 831
  - forward-bias region, 797, 809
  - forward-bias voltage regulator, 814
  - iterative method, 811, 842–843
  - LED, 802
  - load voltage and diode current, 814
  - load-line analysis, 810, 842
  - mechanical analogy, 798
  - negative diode clipper circuit, 831
  - 1N4148 Si switching diode, 797, 798
  - photodiode, 802
  - PIN diode, 802
  - positive diode clipper circuit, 830
  - power electronics, 814
  - rectifiers and regulators, 814
  - reverse-bias region, 797
  - room temperature, 798–800
  - Schottky diode, 801–802
  - Shockley's ideal-diode equation, 798–799
  - shunt voltage regulator, 814
  - switching diode, 797
  - symbol, 797
  - terminal voltage, 797
  - thermal voltage, 799, 800
  - varactor diode, 937, 977
  - voltage reference circuit, 814
  - voltage regulator, 814
  - wave-shaping circuits
    - clammer and multiplier circuit operation, 827
    - diode clamper circuit/DC restorer, 827–828
    - diode voltage doubler and multiplier, 828–830
    - positive, negative and double clipper, 830–832
    - power electronics, 827
    - transfer characteristics, 832–833
  - Zener breakdown voltage, 797
  - Zener diode, 801
- Electronic ignition system, 324, 328
- Electronic switch, 50–51, 643, 645
- Electrostatic discharge (ESD)
  - ESDS device, 263
  - ICs, 263
  - prediction of, 263
- Electrostatics, 3–10
  - conductor, 7–8
  - Coulomb's Law, 9–10
  - electric charge, 3
  - electric field
    - definition, 3
    - laboratory power source, 4
  - electric voltage
    - and electric potential, 4–5
    - vs. ground, 5–7
- Element's polarity, 81
- Encapsulation, 767
- Energy spectral density, 479
- Energy stored in capacitance, 261
- Energy stored in inductance, 282, 283
- Envelope detector circuit, 823
- Equipotential lines, 6
- Equipotential surface, 6, 8
- Equivalent circuit element, 103–104
- Equivalent electric circuits, 99
- Equivalent electric networks, 99

- Equivalent resistance, 102–104, 120  
 Error signal, 230–232  
 Essential mesh, 92  
 Exciting current, 581  
 Exponential diode model, 809
- F**
- Faraday's law  
 current and inductance, 581  
 dot convention, 582  
 ideal open-circuited transformer, 630–631  
 induction, 59, 60, 276  
 primary winding, 580  
 single lossless inductor, 580  
 transformer analysis, 579  
 transformer voltages, 581–582
- Fast Fourier transform (FFT)  
 digital signal processing, 464  
 input sinusoidal signal, 464  
 inverse Fourier transform, 465  
 monotonic frequency data, 465  
 numerical differentiation, 465–466, 480
- Feedback factor, 230  
 Feedback gain, 230  
 Feedback loop, 192, 199  
 Fermi potential, 927
- Filter circuits  
 Bode plot, 441–445, 474–476  
 decibel (dB), 441–444, 474–476  
 first-order filters, 435  
 high-pass, 440–441  
 low-pass, 440  
 phase transfer function, 444–445, 475–476  
 roll-off, 441–444, 474–476
- Filter termination, 439  
 First-order high-pass filter, 441, 448, 466, 480  
 First-order low-pass filter, 443, 448, 449, 455, 480  
 First summing-point constraint, 197–198  
 Fixed resistors, 41–42  
 Flash ADC  
 circuit, 724, 725  
 operation, 725
- Flash memory, 756  
 Flat-band voltage, 928  
 Fluid analogies *See* Hydraulic analogies  
 For loop, 774–776  
 Forbidden state, 655, 670, 672  
 Forced beta, 860  
 Forced current gain, 861  
 Forward current, 71
- Fourier transform  
 bandlimited, 459  
 converting computational electromagnetic solution, 467–472  
 definition, 478–479  
 DFT, 461–462  
 direct, 458  
 Fourier spectrum, 458  
 input pulse signal, 466–467, 480  
 inverse, 458  
 mathematical properties, 460–461, 479  
 rectangular pulse, 459  
 reversal property, 458  
 sampling theorem, 463–464  
 voltage/current signal, 458
- Four-resistor bias configuration, 894  
 Four-terminal NMOS transistor  
 BJT, 922  
 integrated circuits, 922
- Frequency band  
 bandwidth, 451  
 bode plot, 447  
 passband, 443
- Full H-bridge  
 DC motor, 655–656, 681–682  
 transistor switch, 655
- Full-scale output voltage range, 711  
 Full-wave rectifier, 819–820  
 Functions, Arduino language, 765–767  
 Function header, 766  
 Fundamental frequency, 461
- G**
- Gain tolerance, amplifier, 210–211  
 Gauge factor (GF), 44  
 Gauss' theorem, 7
- Generic solar cell  
 application, 170–171, 179, 188  
 maximum power extraction, 185–187  
 nonlinear circuits, 167–168, 187–188  
 solar panels, 179
- Ground reference, 5–6  
 Ground-side switch, 644–646, 651, 660, 679
- H**
- Half H-bridge  
 DC motor, 653–654  
 motor functions, 654  
 switching states, NMOS transistors, 682
- Half-power bandwidth, 491, 492, 497, 503, 520  
 Half-power frequency *See* Filter circuits  
 Half-wave rectifier  
 AC power supply, sinusoidal voltage, 817  
 current-limiting resistor, 818  
 diode rectifier, 818  
 dual supply, 845  
 electronic DC power supplies, 817  
 ideal-diode rectifier, 817, 818  
 plot source and load voltage, 818–819  
 rectified voltage vs. source voltage, 819, 820
- Hard limiter, 832  
 Hardware description language (HDL), 672  
 Harmonic voltage and current  
 AC power supplies, 391  
 AC voltage, 391  
 angular frequency, 391–392

- Harmonic voltage and current (*cont.*)
- benefit, 391
  - complex exponent, 404
  - definition, phasor, 396–398
  - electric circuit, 410
  - electrode, 410
  - frequency, phase and amplitude, 391
  - impedance, 405–407
  - leading and lagging
    - AC signal, 395
    - amplitude and phase, 395
    - frequency, 394
    - phase-shifted AC voltages, 394
    - power electronics, 393
    - zero-phase cosine, 393
  - magnitude
    - impedance, 408–410
    - human body, 410
  - Maxwell's theory, 392
  - measurements, 396
  - operations, phasors and phasor diagram, 401–404
  - and parameters, 391, 392
  - phasors to real signals, 399
  - polar and rectangular forms, 399–401
  - real signals to phasors, 398–399
  - resistance, 405
  - signals, 391
  - steady-state AC circuits, 391
  - steady-state AC voltage, 391
  - steady-state alternating current, 391
- Hexadecimal numbers, 700–702
- High-voltage side, 587
- Howland current source (Howland current pump), 255
- Hydraulic analogies
  - AC circuits, 19
  - DC steady state, 18, 19
  - semiconductor circuit components, 20
- I**
- v-i* characteristics
- circuit elements, 31
  - current source, 55
  - definition, 31
  - c—plot, 53
  - ideal (Shockley) diode, 47
  - ideal diode, 48
  - ideal switch, 35
  - inverse slop, 49
  - Ohm's law, 47
  - ohmic conductor, 47
  - passive circuit elements, 47–48
  - practical current source, 58
  - practical voltage source, 55
  - resistances 34–35
  - solid line, 58
  - static resistance, 48
  - transfer characteristic, 66–67
  - two-terminal switch, 50
  - voltage source, 52–53
- Ideal ammeter, 69
- Ideal-amplifier model, 197–198, 217, 252
- Ideal-diode model, 31, 47, 79
- assumed states, 804, 805, 838–840
  - forward-bias region, 804
  - OFF-diode, 804–806
  - ON-diode, 804–806
  - OR logic gate, 806–807
  - output voltage, 807
  - v-i* characteristics, 804
- Ideal loaded transformer
- circuit symbol, 585
  - contour, 584
  - linear interface, 585
  - power conservation, 585
  - power rating, 587–588
  - vs. real transformer, 586–587, 631–632
  - stored energy, 586
  - terminologies, 587
- Ideal MOS capacitor model, 925
- Ideal open-circuited transformer *See* Faraday's Law
- Ideal transformer equations, 579, 602
- Ideal voltmeter and ammeter, 69–70, 85
- IDFT *See* Inverse discrete Fourier transform (IDFT)
- Impedance matching, 545
- Increment operator, 775
- Incremental resistance, 49
- Independent ideal current source
  - active reference configuration, 55
  - definition, 55
  - symbols, 56–57
  - v-i* characteristic, 56
- Independent ideal voltage source, 52–55
- Inductance
  - dynamic behavior, 281–283
  - self-inductance, 272–273
  - series and parallel, 275–276
  - solenoid with and without magnetic core, 273–275
- Inductor
  - choke, 289
  - fringing effect, 274
  - ideal, 275
  - 1-mH, 276–277
  - physical, 272
- Input and output (I/O) devices, 750
- Input bias current, 219–220
- Instantaneous generator voltage, 60
- Instruction set, 748
- Instrumentation amplifier, 222–229
- Instrumentation transformers, 579, 603
- Integrated circuit (IC), 191, 229
- Integrated development environment (IDE)
  - edit menu, 759
  - features, 758
  - file menu, 759
  - installation, 758

- license agreement, 758
  - sketch menu, 758
  - tools menu, 759
  - USB connection, 757
  - visual representation, 757
  - windows, 758
  - Interface
    - analogRead function, 769
    - Arduino programs, 770
    - IO pins, 769
    - pinMode function, 769
    - PWM signal, 770
  - Internal compensation, 451
  - Internal source resistance, 54, 57
  - Interrupt service routine (ISR), 781
  - Interrupts
    - debounced, 781
    - ISR, 781
    - microprocessor, 781
    - polling, 780
    - queue, 781
    - trigger state, 781
    - volatile, 782
  - Inverse discrete Fourier transform (IDFT), 461
  - Inversion layer of MOS capacitor, 928, 935, 936
  - Inverting amplifier, 203–204
  - Inverting input, 191, 201, 207
  - Inverting Schmitt trigger, 332, 376
  - Isolation transformers, 579
  - ISR *See* Interrupt service routine (ISR)
  - Iterative method for nonlinear circuits
    - definition of, 169
    - explicit iterative scheme, 169
    - implicit iterative scheme, 169
- J**
- Junction FET (JFET), 931
- K**
- Karnaugh maps, 673
  - Kirchhoff's current law (KCL), 93–95
  - Kirchhoff's voltage law (KVL), 14, 95–98
- L**
- Lagging power factor, 536
  - Large-signal BJT circuit model, 866
  - Large-signal circuit model
    - base-bias transistor circuit, 866
    - equivalent circuit model, 866
    - first-order circuit, 866
    - linear current-controlled current source, 866
    - nonlinear voltage-controlled current source, 866
  - Large-signal MOSFET model in saturation
    - digital switching circuits, 939
    - transconductance curve, 940
  - Latch
    - inverters, 673
    - SRAM, 688
    - stable states, 673
  - Laws of Boolean algebra, 668
  - Leading power factor, 537
  - Least significant bit (LSB), 707
  - LED *See* Light-emitting diode (LED)
  - Lenz's law, 630
  - Library, 767
  - Light-emitting diode (LED), 802
  - Line currents, 553
  - Line integral, 5
  - Linear circuit (definition of homogeneity additivity superposition), 116
  - Linear feedback system, 230
  - Linear load, 47, 607
  - Linear oscillators, 330
  - Linear passive circuit element
    - components, 31
    - fixed resistors, 41–42
    - Ohm's law, 33
    - Ohmic conductors, 36–39
    - passive reference configuration, 32–33
    - power delivered, 35–36
    - resistive sensors, 42–45
    - symbols and terminals, 31–32
    - variable resistors (potentiometers), 42
    - voltage across, 32
    - v-i* characteristic (*see v-i* characteristic)
  - Lines of force, 4
  - Line-to-line voltages, 552
  - Line-to-neutral voltages, 547, 552, 557, 575
  - Load cell, 229
  - Load impedances per phase, 549, 573
  - Load line (definition, method of), 167–168
  - Load reflections, 592
  - Load-line analysis
    - actuator device, 951, 952
    - amplifier (*see* MOSFET amplifier) current mirror, 950
    - diode-connected, 950
    - lumped process parameter, 950
    - Ohm's law, 948
    - quadratic equation, 949
  - Load-line method, 810–811, 842
  - Logic inverter, 660–661, 683
  - Loops
    - electric network, 92–93
    - for loop, 774–776
    - while loop, 776, 777
  - Lorentz force, 59, 60, 315, 317
  - Low-frequency asymptotes, 444, 449
  - Low-voltage side, 588, 632
  - LSB *See* Least significant bit (LSB)
  - Lumped process parameter, 934

**M**

- Magnetic field, 271, 272, 299
- Magnetic flux density, 272, 273, 299, 315
- Magnetic induction, 272, 299
- Magnetic permeability of vacuum, 274
- Magnetic radiators
  - application, 638
  - coil array, 622
  - tuned radiators, 623–624
  - two identical, 622–623
  - uncoupled inductors, 623
  - wireless inductive power transfer, 622, 638
- Magnetizing inductance, 581
- Magnetizing reactance, 606, 637
- Magnetostatics
  - Ampere's law, 14–16
  - current-carrying conductor, 12–13
  - current flow model vs. electrostatics, 11–12
  - electric circuit, 13–14
  - electric current, 11
  - electric power transfer, 16–17
- Matched load, 161
- Matched switching transistors, 646
- Matching circuit
  - arbitrary complex impedances, 595
  - real-valued impedances, 593–594
  - transformer, 634
- Material conductivity, 37, 44
- Material resistivity, 37
- Maximum available source current, 54
- Maximum available source power, 54
- Maximum operating frequency, 800
- Maximum power efficiency, 162–163, 184–185
- Maximum power theorem (principle of maximum power transfer), 161, 171
- Maximum power transfer for AC circuits,
  - principle of, 544–545, 572
- Maximum sensitivity of voltage divider circuit, 108–109
- Mechanical analogy, 332
- Memory
  - binary representation, 754
  - bytes, 749
  - data storage methods, 754–755
  - flash, 756
  - organization, 753–755
  - program execution, 749
  - storage, 881
  - types, 755–756
- Mesh analysis (mesh-current analysis), 142
  - linear circuits, 146–147
- Mesheres of electric network, 91–93
- Metal-oxide-semiconductor (MOS) transistors
  - complementary MOS circuits, 645
  - ground-side switch, 645
  - power-side switch, 645
- Metal–semiconductor FET (MESFET), 931
- 1-mH inductor, 276–277
- mho, 33
- Microcontrollers
  - architecture, 747, 748
  - buses, 850–851
  - CPU, 748–749
  - feature, 747
  - hierarchy, 748
  - I/O devices, 747, 850
  - memory, 747, 849
  - timers, 850
  - USART, 851–852
- Miller integrator
  - amplifier circuits, dynamic elements, 290–291
  - compensated, 291–292
- Mobility of charge carriers, 37
- Modulation depth, 824
- MOS field effect transistor (MOSFET)
  - amplifier
    - linear small-signal, 956–957
    - Q-point, 955–956
    - transconductance, 957–958
    - voltage transfer characteristic, 953–954
  - channel, 924
  - CMOS process, 930
  - common-source amplifier (*see* Common-source MOSFET amplifier)
  - DC circuit, 947
  - JFET, 931
  - linear/ohmic subregion, 932
  - load-line method (*see* Load-line analysis)
  - MESFET, 931
  - n and p-channel, 921
  - NMOS
    - capacitor, 924–925
    - and PMOS transistor, 932
  - on-state resistance, 944
  - oxide layer
    - pn-junction depletion layer, 926
    - SiO<sub>2</sub>, 926
  - parameter extraction, 943–944,
  - PMOS transistor, 929–930, 939
  - process transconductance parameter, 934
  - resistor-switch model, 944
  - saturation current, 936
  - saturation region, 935–937
  - semiconductor body
    - Fermi potential, 927
    - inversion layer, 927, 928
    - mass-action law, 927
  - simplifier transistor circuit, 933
  - terminal voltages and currents
    - drain-source voltage, 923
    - gate-drain voltage, 923
    - gate-source voltage, 923
  - threshold voltage, , 921–933
  - transconductance parameter
    - curve, 940
    - lumped process parameter, 934
  - transistors, 646

turn-on resistance, 934, 942–944, 968  
*v-i* dependencies, 937–938  
 work function difference, 928, 929  
 Motor control states (forward mode), 650, 652  
 Motor speed controller, 650  
 Motor switching  
   forward mode, 650  
   free run to stop, 650  
   motor brake, 650  
   reverse mode, 650  
 Multiwinding transformer, 599–600, 636  
 Mutual inductance, 272–273

## N

NAND gate  
   vs. input voltages, 662  
   symbol, 663  
   three inputs, 664  
 n-channel metal-oxide-semiconductor field-effect (NMOS) transistor, 20  
 n-channel MOSFET, 653  
 Near-field communication (NFC), 506  
 Near-field wireless link, 506, 510–511, 522  
 Negative clipper, 831  
 Negative equivalent (Thévenin) resistance, 182  
   construction and use, 158  
   dependent source, 158  
   voltage-controlled voltage source, 158  
 Negative feedback  
   amplifier's stability, 199  
   idea of, 199  
   summing-point constraints, 199–201  
 Negative phase sequence, 524, 573  
 Negative temperature coefficient (NTC), 43  
 Neper (Np), 348, 358  
 Neutral wire, 553–555, 573–576  
 NFC *See* Near-field communication (NFC)  
 NMOS transistor  
   channel inversion, 924  
   threshold voltage, 928  
 Nodal analysis, 142, 176–177  
   circuit current  $I$ , 176  
   linear circuits, 146–148  
   supply current  $I$ , 176  
 Nodes of electric network, 92–94  
 Noise signals, 530  
 Nonideal low-frequency transformer, 617  
 Nonideal transformer model  
   harmonic source and linear load, 607  
   impedance load, 607  
   input voltage, 609  
   load current, 607  
   load voltage, 607  
   power factor, 609  
   rms values, 606  
 Non-inverting amplifier, 201–203

Non-inverting input, 192, 193  
 Non-inverting Schmitt trigger, 332, 376  
 Nonlinear circuits, 167–168  
   definition of linearization dynamic/small-signal resistance, 116  
 Nonlinear passive circuit elements, load, 46  
 Non-ohmic circuit elements, 46  
 Non-reference, 141  
 Nonvolatile memory, 755  
 NOR gate, 661  
   vs. input voltages, 660  
   three inputs, 664  
 NOT gate, 660–661, 663, 665, 666  
 n-type/n-channel MOS transistor (NMOS)  
   control voltage, 646  
   ground-side switch, 645  
   intrinsic threshold voltage, 648  
   load current, 647  
   metal electrodes, 647  
   threshold voltage, 647  
 Nyquist rate  
   minimum acceptable sampling rate, 723  
   modulation theory, 723  
   Nyquist-Shannon sampling theorem, 723  
   oversampling and undersampling, 723  
   sampling frequency, 723  
 Nyquist-Shannon sampling theorem, 723

## O

Objects, 768, 769  
 Octave, 443, 474  
 Offset-null terminals, 192, 218  
 Ohm's law, 35, 36, 39, 47, 49, 67  
   resistance and conductance, 33  
 Ohmic conductor, 36–39  
 One-port network, 99  
 Open-circuit, 34  
   small-signal voltage gain, 956, 958  
   source voltage, 54, 57, 60, 65, 67, 83  
   voltage gain, 192, 232, 889, 891, 895  
 Open-loop AC gain, 453–454, 477  
 Open-loop configuration, 192, 199  
 Open-loop voltage gain, 192  
 Operating point, 49, 50  
 Operational amplifier  
   application, 194–195  
   bandwidth, 455–456, 477–478  
   closed-loop AC gain, 454–455, 477  
   definition, 191  
   frequency bandwidth, 451, 456–457, 478  
   open-circuit/open-loop voltage gain, 192  
   open-loop AC gain, 453–454, 477  
   open-loop amplifier gain, 451, 477  
   open-loop gain behavior, 451–452  
   power rails and voltage transfer characteristic, 193, 194  
   symbol and terminals, 191–192

- Operational amplifier (*cont.*)  
 unity-gain bandwidth vs. gain-bandwidth product,  
 452–453, 477
- OR gate, 661–662, 669
- Output resistance, 863, 873, 889, 891, 895, 896
- Output terminal, 192, 196
- P**
- Parallel battery bank, 101
- Parallel connection, 103
- Parallel data transmission, 751
- Parallel digital output voltage, 693
- Parallel-plate capacitor  
 application, 267–269  
 capacitive touchscreens, 270–271  
 capacitor marking, 269–270  
 ceramic capacitors, 269  
 circuit symbol, 266–267, 275–276  
 dielectric permittivity of vacuum, 265  
 electrolytic capacitors, 269  
 fringing effect, 265  
 inductor marking, 277  
 mutual-capacitance method, 271–273  
 opposite charge  $-Q$ , 264  
 self-capacitance method, 270–271  
 solenoid with and without magnetic core, 273–275  
 static capacitance, 266  
 total charge  $+Q$ , 264  
 touch screens, 265
- Parallel resonant RLC circuit  
 amplitude, 493  
 circuit voltage, 494  
 duality, 495, 519, 520  
 parallel RLC tank circuit, 493  
 partial time constants, 493  
 phasor representation, 493  
 $Q$ -factor, 494  
 resonance condition, 493  
 resonant frequency, 493–494  
 resonant phasor currents, 495  
 second-order RLC filters, 504–505
- Parallel vs. serial representation, 693, 694
- Parseval's theorem, 479
- Passive linear circuit elements, 278
- Passive reference configuration, 32–33
- p-channel MOSFET, 929, 944
- Peak detector circuit, 823
- Peltier-Seebeck effect, 44
- Peripherals, 750
- Per-phase solution, 553
- PFC capacitor, 539–541, 543
- Phase impedances, 549, 557, 575
- Phase voltages, 547–549, 572, 573
- Photocell, 43
- Photoresistor, 44, 45
- Piecewise-linear diode model, 801, 816, 817
- PMOS transistor, 929–930
- Polarity  
 AC source, 67  
 active reference configuration, 52, 56  
 independent, 52  
 voltage, 32, 34
- Polling, 780
- Positive feedback, 330, 335, 372
- Positive phase sequence, 548, 549, 551, 556, 560
- Postfilter, 710
- Potential transformers, 603
- Potentiometer, 42
- Potentiometric position sensor, 44–45
- Power angle, 531–532, 569
- Power conservation law for electric networks, 99
- Power factor correction  
 application, 542  
 average load power, 541  
 capacitance value, 540  
 capacitor, 539  
 current amplitude, 541  
 impedance, 540  
 load impedance, 542  
 modified load, 539  
 power angle, 539  
 reactive load power, 540  
 RLC circuit, 539  
 shunt capacitor, 539, 540
- Power rails, 193
- Power-related networking theorems, 98–99
- Power-side switch, 644–646, 679, 884
- Power switching circuits  
 DC motor, 651–652  
 full H-bridge, 655–657  
 half H-bridge, 653–654  
 one-quadrant switch, 652–653  
 PWM motor controller, 657–659  
 resistive load, 651  
 switching quadrants, 650–651
- Power terminals, 230
- Power triangle, 570–571  
 inductive and capacitive load, 535, 536  
 whip antenna, 537
- Poynting vector, 17
- Practical current source  
 definition, 58  
 open-circuit voltage, 57  
 short-circuit current, 57  
 $v$ - $i$  characteristic, 58
- Practical voltage source, 54–55
- Primitive data types, 762
- Process transconductance parameter, 934
- Product-of-sums approach, 672–673
- Proximity sensors, 511–516, 520, 521
- P-type/p-channel MOS transistor (PMOS), 646  
 control voltage, 646  
 intrinsic threshold voltage, 648

- output voltages, 648–649
  - power-side, 653
  - power-side switch, 679
  - threshold voltage, 646
  - Pull-down switch *See* Ground-side switch
  - Pull-up switch *See* Power-side switch
  - Pulse-width modulation (PWM), 716, 768, 782, 783
    - average supply voltage, 657
    - commercial controllers, 658
    - duty cycle, 657
    - motor controller, 657–659, 682
    - realization, 658, 659
    - supply voltage, motor, 657
    - voltage form, 657–659
  - PWM *See* Pulse-width modulation (PWM)
- Q**
- Quality factor
    - constant, 489
    - definition, resonant frequency, 488
    - inductor and capacitor, 489
    - maximum amplitude, 489
    - mechanical resonator, 489
    - series resonant LC circuit, 490
    - series resonant RLC circuit, 491
  - Quality factor of series resonant RLC circuit, 488
  - Quantization error, 727
  - Quiescent-point (Q-point), 49, 810, 812
    - NMOS amplifier, 955
    - parameters, 891
- R**
- Radiation resistance, 47
  - Radio-frequency (RF)
    - inductor choke, 289
    - power, 823
  - Rail-to-rail amplifiers, 194
  - Reactive power, 535
  - Real transformer, 604
    - equivalent circuit values, 606
    - model parameters and extraction, 604–606
    - nonideal low-frequency
      - core loss resistance, 604
      - leakage resistance, 604
      - leakage inductance, 604
      - ohmic resistance, 604
      - Steinmetz model, 604
  - Receiver circuit, 522
    - Faraday's law, 508
    - open-circuit voltage, 509, 510
    - operating frequency, 510
    - quality factor, nonideal inductor, 510
    - voltage multiplier, 510
  - Reconstruction filter, 710
  - Rectangle rule, 461
  - Reduction of resistive networks, 104–105
  - Relative magnetic permeability, 275
  - Replacing a node by a loop, 120
  - Resistive sensors, 42–45
  - Resistor, 40
    - ECE laboratory kit, 77
    - fixed, 41–42
    - photoresistor, 44
    - thermal, 42
    - variable, 42
  - Resolution voltage, 708–710
  - Return current and ground, 71
  - Reversal property, 458, 479
  - Riemann sum approximation, 461
  - RL filter circuits, 448–450, 476
  - rms voltage
    - AC signals, 567
    - application, 567
    - DC voltage, 530
    - root-mean-square value, 530
    - sawtooth/triangular wave, 530
    - single-frequency voltage signals, 530
  - Rotating magnetic field, 550
  - Rotor, 550
  - R/2R ladder DAC, 714–715
  - R-2R ladder network, 157
- T**
- T and  $\Pi$  networks, 121–122
  - Telephone hybrid circuit, 600
  - Tellegen's theorem, 98
  - Thermistor constant, 43
  - Thermistor equation, 43
  - Thermocouple, 43
  - Thévenin equivalent, 153, 155, 158, 162, 167, 181
  - Thévenin's and Norton's theorems, 153–182
  - Three-terminal MOSFET, 922, 923, 932
  - Three-terminal networks, 119
  - Threshold voltages, 332
  - Timing diagram, 697, 698
  - T network, 122, 132
  - T pad, 122
  - Transconductance, 66, 67
    - amplifier, 65, 233
    - curve, 940
  - Transfer characteristic, 66–67
  - Transfer resistor, 854, 862
  - Transient circuit, 284
  - Transient RC circuit
    - capacitor, 310
    - digital memory cell, 317–318
    - electromagnetic railgun, 314–316, 369
    - energy-accumulating capacitor circuit
      - forced response, 319
      - resistor voltage, 319
      - source voltage, 320
      - Thévenin resistance, 318
    - energy consideration, 313

- Transient RC circuit (*cont.*)
    - energy-release capacitor circuit
      - electromagnetic material processing, 312
      - load resistor, 310
      - time/relaxation constant, 311
    - fluid mechanics analogy, 314
    - static/dynamic circuit, 310
    - time constant, 312–313
  - Transient RL circuit
    - energy-accumulating capacitor circuit
      - charging, 325
      - inductor/resistor voltages, 326
      - inhomogeneous, 325
      - mH inductor, 326
      - supply current, 327
      - voltages and currents, 321
      - zero inductor current, 326
    - energy-release inductor circuit
      - charged, 321
      - current source, 321
      - dynamic circuit, 321
      - inductor, 321, 322
      - magnetic-field energy, 321
      - supply current, 322
      - time/relaxation constant, 322
    - inductor current
      - continuous function, 324
      - finite magnetic-field energy, 324
      - fluid mechanics analogy, 324, 325
      - independent function, 324
      - inductor inertia, 324
    - laboratory ignition circuit, 328–329
    - static/dynamic circuit, 321
    - voltage supply, 327
  - Transistor circuit analysis
    - collector and base resistances, 871
    - current-controlled current source model, 872, 873
  - Transistor test circuits, 856, 866, 871
  - Transistor threshold voltage
    - digital circuits, 647
    - switching behavior, 646
  - Transmission line, 14
  - Transmitter circuit, 522
    - magnetic field, 507
    - operation frequency, 507
    - phasor method, 507
    - quality factor, 507
    - series capacitor, 507
  - Transmitting antenna, 163
  - Transresistance amplifier, 65, 233
  - Triode region, MOSFET
    - electron surface mobility, 934
    - lumped process parameter, 934
    - process transconductance parameter, 934
    - turn-on resistance, 934
  - Tri-state buffer, 704–705
  - Tri-state digital voltage
    - buffer, 704
    - components, 705
  - True power, 544
  - Truth table
    - AND gate, 666
    - logic circuit, 661, 670–671
    - NAND gate, 665
    - OR gate, 666
  - Tuning diode, 800
  - Two coupled inductors
    - circuit analysis, 607
    - circuit symbol, 613
  - Two-port networks, 121–122
  - Two-terminal network (definition of input port
    - output port), 119
  - Two-terminal switch, 50
  - Typecasting, 764
- U**
- Undamped resonant frequency, 348, 352, 381, 384, 385
  - Underdamped circuit, 357, 360
  - Unidirectional switch, 50
  - Unity common-mode gain stage, 227
  - Universal synchronous/asynchronous receiver/transmitter (USART)
    - CPU and external serial devices, 752
    - parallel data transmission, 751
    - serial data transmission, 751
  - USART *See* Universal synchronous/asynchronous receiver/transmitter (USART)
- V**
- Variable resistor, 42
  - Velocity saturation region, 936
  - Very high frequencies, 285
  - Virtual-ground circuit, 220–221
  - Virtual ground of dual-polarity power supply, 101
  - Virtual-ground (integrated) circuit, 221
  - Volatile memory, 755
  - Voltage amplifier, 65
  - Voltage-controlled current source, 65–66
  - Voltage-controlled voltage source, 65
  - Voltage difference, 5, 32, 52, 61
  - Voltage divider circuit, 105–107
  - Voltage division rule, 107
  - Voltage drop, 5, 32, 37, 56
    - absolute voltage, 72–74
  - Voltage follower (buffer) amplifier, 204–205
  - Voltage polarity, 31, 32, 55, 582, 613
  - Voltage transfer characteristic, 193, 953, 954
  - Volt-amperes (VA), 535
  - Volt-amperes reactive (VAR), 535
- W**
- Wattmeter, 538
  - Wattmeter current coil, 538
  - Wheatstone bridge (definition of difference signal
    - difference voltage balanced), 113–115

- While loop, 776, 777
  - Wireless inductive power transfer
    - coaxial coupled inductors, 619
    - coil configuration, 618
    - data transfer, 618
    - finite magnetic core, 621
    - magnetic near-field calculations, 620
    - MATLAB script, 621
    - mutual inductance, 620
    - RFID, 619
    - transmission frequency, 620
  - Work function difference, 928
  - wye-connected load, 549, 560
  - Wye-connected source, 549, 560, 561
  - Wye-wye distribution system, 552
  - Wye/Y configuration, 549
- X**
- XOR gate, 670
- Y**
- Y and  $\Delta$  Networks, 119, 121
  - Y to  $\Delta$  transformation, 121
- Z**
- Zener diode
    - piecewise-linear, 816–817
    - shunt voltage regulator, 815–817
    - voltage regulator, 843, 844
  - Zero-level detector, 195, 240