

Index

A

Acceptor, 35
Accelerometer, 129, 131
Active device interface (with a bipolar transistor), 104, 108, 113
Active region, 44, 46, 48
Adder, 201, 228, 231, 232, 234, 235, 238, 241, 257
Address decoder, 276–279
Analog microphone, 183
Analog-to-Digital Converter (ADC), 157–160, 163, 165–167, 183, 185, 191
AND gate, 202, 203, 205, 210–212, 222, 225, 231, 238, 239
Array multiplier, 201, 244–246
As atom, 34

B

Barrel shifter, 201, 241–244
Base current, 43–45, 90
Base-emitter voltage, 45
B atom, 34
Bipolar transistor, 43, 46, 47, 49, 104, 108, 109, 112–115, 118–120
Block diagram, 264, 269, 279, 283
Boltzmann constant, 37
Boolean algebra, 208
Breakdown voltage, 189
Buffer, 204, 207, 247, 276
Buzzer, 177, 178

C

Capacitance, 68, 76, 131
Capacitor, 2–4, 10, 13, 14
Carry-look-ahead adder, 201, 233, 235, 238–240
Carry-select adder, 201, 229, 234, 235, 239
Clock, 201, 247–257, 259–263, 273, 274, 279, 280, 282
CMOS inverter, 62, 63
CMOS NAND logic gate, 63, 64
CMOS NOR logic gate, 65, 66
CMOS-TTL interface, 118, 119
Collector, 43–45
Collector-base voltage, 45
Collector current, 90, 91, 94

Collector-emitter voltage, 44

Combinational logic, 201, 214, 223, 225, 232, 249, 250, 252–255, 263, 267, 268
Complementary MOS (CMOS), 62
Complemented logic gate, 205
Complex CMOS logic gate implementation, 66
Complex plane, 20, 21, 23, 26
Conduction band (EC), 35, 123, 125, 127
Constant coefficient differential equation, 4, 15
Controller design, 279, 282
Counter, 194–197, 201, 262, 263, 272–275, 279, 280, 282
Counter-decoder design, 201, 272–275, 282, 283, 286
Crystalline structure, 33–35
Current gain, 45, 52
Current-voltage characteristics, 58, 60
Cut-off region, 44, 46

D

Data-path, 202, 256, 279, 280, 282, 283
DC motor control, 178, 181
Decoder, 201, 225, 275, 283
De Morgan's theorem, 210
Denominator, 22, 24
D flip-flop, 250–253
Difference amplifier, 138, 142
Digital-to-Analog Converter (DAC), 162, 163, 166, 169, 170
Diode, 37–40, 42, 89–91, 94, 97, 99–101, 116, 117, 120
D latch, 247, 248, 250
Down-rounding, 163, 165, 167
Drain current (I_D), 57, 59
Drain-source saturation voltage (V_{DSAT}), 57, 59–61
Drain-source voltage (V_{DS}), 57–60, 83

E

Effective resistance, 198
Electromechanical, 175, 176
Electron, 33–36, 58, 123–125, 127, 129, 132
Electron mobility (μ_N), 76
Embedded system, 123, 127, 132
Emitter, 43–45
Emitter current, 90, 91, 99, 100

Encoder, 201, 223, 224
 Energy band bending, 127
 Energy band gap (EG), 35
 Equivalent circuit, 10, 13, 15, 16, 22, 24, 43, 124, 128
 Equivalent resistor, 40, 52
 Exclusive NOR gate, 65
 Exclusive OR gate, 204
 Exponential, 37, 44
 Extrinsic semiconductor, 34, 35

F

Fall delay, 73, 74
 Fall time, 72–74, 76
 Fermi level (E_F), 35, 36, 125
 First-order passive circuits, 3
 Flash-type ADC, 160–162, 165
 Forward-bias, 51
 Forward voltage, 36–38
 4-1 multiplexer, 222
 4-1 MUX, 222, 223
 Free electron, 34, 35
 Frequency domain analysis, 1, 19, 24
 Front-end electronics, 183, 185, 189, 194, 196, 201
 Full adder, 229, 234, 246
 Full-wave rectifier, 40, 41

G

Galvanometric voltage drop, 123, 124
 Gate, 57, 59, 62, 63, 65–68, 73, 74, 76–78, 201–208, 231, 247, 252
 Gate oxide capacitance (C_{OX}), 58, 60
 Gate-source voltage (V_{GS}), 62
 General solution, 4, 7

H

Half adder, 228
 Half-wave rectifier, 38, 39, 41
 Hall-effect device, 132, 133, 182, 183, 196
 Hall-effect sensor, 196
 Hall-effect switch, 196
 Hall-effect tachometer, 196
 Hall voltage (V_H), 132, 182
 Hardware, 191
 Hold time, 251, 254, 255
 Hold violation, 255–258
 Hole, 36, 60, 125, 127
 Hole mobility (μ_p), 76

I

ID-VDS curve, 59
 Inductance, 2, 14, 24, 28, 31, 198
 Inductor, 2, 6, 14, 15
 Initial condition, 8, 10, 11, 15, 16

Input current, 116, 119, 121
 Input Current High (IIH), 103, 111
 Input Current Low (IIL), 102, 111
 Input current measurement, 102, 103
 Input impedance ($Z_{IN}(s)$), 13, 135, 138
 Input resistance (R_{IN}), 153
 Input voltage ($V_{IN}(s)$), 13, 90, 91, 108, 111, 116–119
 Input Voltage High (VIH), 103, 111
 Input Voltage Low (VIL), 102, 111
 Input voltage measurement, 103
 Instability, 20
 Intrinsic, 33, 35
 Inverter, 205, 207, 208, 222, 247, 257
 Inverting amplifier, 135–137, 142, 144
 Isolation circuit, 138

J

Junction, 36, 37, 43–46

K

Karnaugh map, 201, 214
 Kirchoff's voltage law, 3, 6, 10, 14
 K-map, 214–219, 221, 224, 227, 266, 267, 270, 271, 274

L

Ladder-type DAC, 170, 171
 Laplace transform, 1–4, 15, 22, 23
 Leakage current, 37, 44
 Light Emitting Diode (LED), 42, 176, 177, 183
 Light level measurement, 190, 191
 Linear shifter, 241, 242
 Load line, 47–50
 Logic gate, 201, 204, 205, 208, 211, 257

M

Magnetic field, 132, 133
 Magnetic tachometer, 196
 Mealy machine, 268
 Memory, 201, 247, 249, 276–284
 Minimization, 201, 214, 216, 217
 Moore machine, 263–268, 270, 283
 2-1 multiplexer, 220
 Multiplier, 245
 2-1 MUX, 220, 221, 234, 239, 241, 257, 259, 275

N

NAND gate, 205, 223, 257, 258
 Natural frequency, 12–15, 19
 N-channel MOSFET (NMOSFET), 57–59, 65
 Next state, 263, 264, 266, 268
 NMOS transistor, 58, 59, 62, 63, 65–67, 69, 75, 76
 NMOS transistor threshold voltage (V_{TN}), 58

NMOS tree, 63, 65–67, 69
 Non-inverting amplifier, 137, 145
 NOR gate, 206
 NPN transistor, 43, 44, 48, 108, 109, 118, 120
 N-type semiconductor, 35, 36, 125, 127
 Numerator, 13

O

One bit full adder, 226–229, 232, 257
 One-bit half adder, 228, 229
 Open-collector, 93–96
 Operational amplifier (Opamp), 135, 137, 142, 144–146, 150, 151
 Optoelectronic tachometer, 194–196
 Opto-isolator, 176–178, 181
 OR gate, 203, 210–212, 222, 223, 232, 239
 Oscillation, 18, 21
 Oscillatory, 20, 21, 27
 Output, 202–208, 211, 212, 214, 215, 217, 218, 220, 221, 223, 225–227, 229, 232, 234, 241–243, 246, 248, 250, 251, 257, 259, 261–264, 266, 268, 269, 272–276, 282, 283, 285
 Output current, 91, 108, 116, 119, 121
 Output Current High (IOH), 91–94, 97, 104, 111–113
 Output Current Low (IOL), 91–95, 103, 105, 112
 Output current measurement, 103
 Output impedance, 135, 151
 Output I-V characteristics, 37, 46, 48, 49
 Output voltage, 94, 101, 117, 118, 120
 Output Voltage High (VOH), 91, 104, 112
 Output Voltage Low (VOL), 94, 103
 Output voltage measurement, 103, 104

P

Parallel plates, 131
 Particular solution, 4, 7
 Passive device interface (with a resistor), 104, 107, 116
 Passive elements, 12
 Passive network, 14, 19–21
 P-channel MOSFET (PMOSFET), 59–61
 Photo detector, 191, 192
 Photodiode, 125–128
 Photon, 125, 129
 Photo-resistor, 129
 Photo-transistor, 176, 177
 Photovoltaic voltage drop, 128
 Piezoelectric, 129, 130
 PMOS transistor, 60–65, 67–69, 76
 PMOS transistor threshold voltage (V_{TP}), 60
 PMOS tree, 63–66, 69
 PN junction, 36, 37
 PNP transistor, 43
 Poles, 19–21, 25–27

POS, 212, 214, 215, 217–219, 222, 229
 Power supply voltage (V_{CC}), 47, 90, 91, 94, 104, 107, 111, 117
 Power supply voltage (V_{DD}), 58, 61, 63
 Present state, 263, 264, 266, 268, 269, 272, 282, 283
 Product of sums, 212
 P-type semiconductor, 35, 36, 125–127
 Pull-down resistor, 116, 117
 Pull-up resistor, 94, 104–108
 Pulse Width Modulation (PWM) circuit, 178–181

R

Ramp-type ADC, 162–165
 Read enable, 276
 Rectifying diode, 38
 Reference signal, 138
 Reference voltage, 158, 160
 Register, 201, 259–262, 276, 279
 Relay, 175, 176
 Resistor, 1–3, 6, 14
 Reverse-bias, 37, 44
 Reverse voltage, 36, 37
 Ripple-carry adder, 201, 229, 230, 234
 Rise delay, 73
 Rise time, 72

S

Sample and hold, 157, 160, 163
 Sampling, 157–160
 Saturation, 90, 94, 95, 97, 98, 100, 101, 113, 114, 118
 Saturation region, 44, 45
 Schmitt trigger, 147–150
 2s complement addition, 240, 241
 Semiconductor, 33–35
 Sensor, 127, 135–145
 Sequential logic, 201, 279
 Servo control, 182
 Set-up slack, 258
 Set-up time, 248, 251, 252, 254, 255
 Set-up violation, 254–256
 Shifter, 241
 Shift register, 201, 261, 262
 Silicon, 33, 38
 Sinusoidal, 38–41
 Solar cell, 127, 128
 Source, 57, 59–61
 Square waveform generator, 150–152
 Stability, 19, 22–24
 State diagram, 263–265, 268, 269, 272–274
 State machine, 201, 263, 267, 268, 272–274, 282, 283
 State table, 264–266, 269, 270, 274
 Subtractor, 201, 241
 Successive approximation, 165, 166, 168

Successive approximation ADC, 165, 167
Summation amplifier, 141
Sum of products (SOP), 212, 214–216, 218–222, 224, 227, 266, 267, 270, 271

T

Temperature measurement, 186, 187
Tensile stress, 129, 130
Thermocouple, 123, 124, 185–187
Time constant, 13, 14, 62
Time-domain analysis, 1, 22, 23
Timing diagram, 201, 202, 249, 252, 254–256, 258–263, 273–275, 279–283
Timing methodology, 250, 253
Timing violations, 201, 254
Transfer function, 19, 24
Transistor length, 76
Transistor-Transistor Logic (TTL), 89, 90, 92, 102, 104–106, 108–113, 115, 116, 118–120
Transistor width, 75, 76
Transition table, 266, 269, 270, 274
Trans-resistance amplifier, 144, 145
Tri-state, 207, 208, 247, 251, 276
Truth table, 201–203, 205, 206, 211–217, 224, 225, 227, 276, 277
TTL-CMOS interface, 104, 107–109
TTL inverter, 89–96, 105, 107–109
TTL NAND logic gate, 97–99
TTL NOR logic gate, 99–102

U

Unity gain, 138, 145
Up-counter, 162, 163, 165
Up-rounding, 163, 165–167

V

Valence band (E_V), 36, 125, 127
Voltage amplifier, 135, 137, 139, 142, 145
Voltage comparator, 146, 147

W

Waveform, 5, 6, 8, 9, 11, 12, 17–21, 27
Weighted sum DAC, 169
Work function, 123, 124
Worst-case charge path, 64, 72
Worst-case discharge path, 65, 72
Write enable, 259, 276

X

XNOR gate, 206, 207
XOR gate, 204, 206, 231, 232

Z

Zener diode, 42
Zeros, 4, 19, 22, 24