 


### 4.1 TTL Inverter

Transistor-Transistor-Logic (TTL) is still used in limited capacity in discrete ICs due to its ability to deliver (or sink) large currents. However, power consumption, slow speed and the cost of fabrication are its main drawbacks. All TTL logic gates are composed of three stages. The simplest TTL logic gate, TTL inverter, is shown in Fig. 4.1.



**Fig. 4.1** A simplified TTL inverter

The input stage of this gate contains only a single transistor,  $Q_1$ . This transistor is equivalent to two back-to-back diodes as shown in the inset of Fig. 4.1, and this


configuration directs the current flow either towards the IN terminal or towards the control stage to activate  $Q_2$  depending on the logic value at the input.

The control stage contains  $Q_2$ . Its function is to supply part of its emitter current to saturate  $Q_3$  or turn off this transistor.

The output stage, also called totem-pole configuration, consists of  $Q_3$  and  $Q_4$ .  $Q_3$  absorbs all the current (sink current) from an output load.  $Q_4$  supplies current (source current) to an output load. Supply voltage for any commercially available TTL stage is usually 5 V.

**TTL Inverter When IN = 5 V**

When the input voltage at the IN node is raised to 5 V, there will be no voltage drop across the diode,  $D_1$  (corresponding to the emitter-base junction of  $Q_1$ ). As a result,  $D_1$  turns off as shown in Fig. 4.2.

 

**Fig. 4.2** Currents and voltages of the TTL inverter when IN = logic 1

Therefore, the current from the voltage supply,  $V_{CC}$ , directly flows into the base of  $Q_2$  through  $D_2$  (corresponding to the collector-base junction of  $Q_1$ ), forming the base current for  $Q_2$ ,  $I_{B2}$ , and driving this transistor into saturation.


When  $Q_2$  is in the saturation region, its collector current,  $I_{C2}$ , combines with  $I_{B2}$ , and forms the emitter current for  $Q_2$ ,  $I_{E2} = I_{B2} + I_{C2}$ . The majority of  $I_{E2}$  flows into the base of  $Q_3$  and drives this transistor into saturation. The remaining part of  $I_{E2}$  flows through  $R_3$ , and biases the base-emitter junction of  $Q_3$  with 0.8 V.

As a result of this scenario, the voltage drop between the base of  $Q_4$  and the output terminal becomes  $0.2 + 0.6 = 0.8$  V. However, this potential difference is not sufficient to turn on  $Q_4$  and the diode at the output stage simultaneously since they require at least  $0.8 + 0.7 = 1.5$  V. Thus,  $Q_4$  turns off.

As a result,  $I_{C3}$  becomes the “sink” current and absorbs all the output current from an external resistor,  $R_L$ , as shown in Fig. 4.2. This current is also called  $I_{OL}$ , corresponding to the low output current when the output is equal to  $V_{OL}$ .

### TTL Inverter When $I_N = 0$ V

When input voltage at  $I_N$  is lowered to 0 V, current flows through the diode,  $D_1$  (corresponding to the emitter-base junction of  $Q_1$ ), and turns on the diode. The voltage developed across this diode, 0.7 V, then becomes equal to the sum of the voltage drops across  $D_2$  (corresponding base-collector junction of  $Q_1$ ), the base-emitter junction of  $Q_2$  and the base-emitter junction of  $Q_3$ . However, 0.7 V is not enough to saturate the transistors,  $Q_2$  and  $Q_3$ , and turn on the diode at the same time as shown in Fig. 4.3.

 

**Fig. 4.3** Currents and voltages of the TTL inverter when  $I_N = \text{logic } 0$


Since  $Q_2$  stays off, the supply current,  $I_{B4}$ , flows into the base of  $Q_4$  and saturates this transistor. The collector current of  $Q_4$ ,  $I_{C4}$ , combines with  $I_{B4}$  to form the emitter current for  $Q_4$ ,  $I_{E4}$ . This current becomes the “source” current and flows into an external load resistor,  $R_L$ , as shown in Fig. 4.3. This current is also called  $I_{OH}$ , corresponding to the high output voltage,  $V_{OH}$ . However,  $V_{OH}$  never reaches the full supply voltage of 5 V, but stays around 3.5 V due to the combined voltage drop between  $V_{CC}$  and the OUT terminal, namely  $R_4 I_{C4} + 0.2 + 0.7 \approx 1.5$  V.

**Example 4.1** There are two ways for a TTL inverter to drive an LED. The circuit configuration depends on the current requirement of the LED, and the relative values of  $I_{OH}$  and

$I_{OL}$  given in the manufacturer's datasheet. If the LED requires high current, and  $I_{OH}$  happens to be much higher than  $I_{OL}$  in the datasheet, then the best way to connect the LED is between the output terminal and the ground as shown in Fig. 4.4. As a result,  $I_{OH}$  is used to turn on the LED.

The series resistance,  $R_L$ , is computed as follows:

$$R_L = \frac{(V_{OH} - V_{LED})}{I_{OH}} \quad (4.1)$$

 

**Fig. 4.4** TTL inverter driving LED if  $I_{OH}$  is much greater than  $I_{OL}$


In this equation,  $V_{LED}$  is the voltage drop across the LED.

If the LED requires high current and the TTL manufacturer's datasheet specifies that  $I_{OL}$  is much higher than  $I_{OH}$ , then the better circuit configuration would be to connect the LED between the supply voltage and the  $OUT$  terminal as shown in Fig. 4.5. That way,  $I_{OL}$  of the TTL inverter supplies all the current the LED needs.

This time,  $R_L$  becomes:

$$R_L = \frac{(V_{CC} - V_{LED} - V_{OL})}{I_{OL}} \quad (4.2)$$


If the LED's current requirement is low and comparable to  $I_{OH}$  or  $I_{OL}$ , then either circuit configuration in Figs. 4.4 or 4.5 can be used to turn on the LED.

 

**Fig. 4.5** TTL inverter driving LED if  $I_{OL}$  is much greater than  $I_{OH}$

## 4.2 TTL Inverter with Open Collector

If the TTL inverter's  $I_{OL}$  is much higher than  $I_{OH}$ , the output transistor  $Q_4$  may not be necessary at all to operate an LED or some other two-terminal device. This reduces the overall device count in the inverter and forms a much simpler circuit called open-collector inverter as shown in Fig. 4.6. With open-collector configuration, the high logic level also reaches to the full voltage supply value of 5 V instead of staying at 3.5 V.

 


**Fig. 4.6** Open-collector TTL inverter

The operation of open-collector inverter is similar to the operation of a common TTL inverter. However, the open collector of  $Q_3$  will always need a pull-up resistor to operate properly.


Figure 4.7 describes the operation of this logic gate with a pull-up resistor when IN is connected to 5 V. The diode corresponding to the emitter-base junction of  $Q_1$  turns off because there is 0 V across this junction.  $Q_2$  goes into the saturation region with a current flowing in its base,  $I_{B2}$ . A large portion of  $Q_2$ 's emitter saturation current,  $I_{E2}$ , also flows into the base of  $Q_3$  and causes this transistor to go into saturation provided that  $Q_3$  is biased properly with an external load resistance,  $R_L$ . The output voltage becomes  $V_{OL}$ , which is in the order of 0.2 V.  $I_{OL}$  becomes the collector current of  $Q_3$ .  $R_L$  is determined in terms of  $V_{OL}$  and  $I_{OL}$  according to the following equation:

$$R_L = \frac{(V_{CC} - V_{OL})}{I_{OL}} \quad (4.3)$$

 

**Fig. 4.7** Open-collector TTL inverter driving a CMOS gate when IN = logic 1

When  $IN = 0$  V, the diode corresponding to the emitter-base junction of  $Q_1$  turns on as shown in Fig. 4.8. However, the base of  $Q_1$ , now standing at 0.7 V, will not be sufficient to turn on the transistors,  $Q_2$ ,  $Q_3$  and the diode corresponding to the collector-base of  $Q_1$ . The output node is pulled up to  $V_{CC}$ .  $I_{OH}$  through  $R_L$  becomes 0 A.

 

**Fig. 4.8** Open-collector TTL inverter driving a CMOS gate when  $IN = \text{logic } 0$

**Example 4.2** Assume the output of the open-collector inverter in Fig. 4.7 includes an LED in series with  $R_L$ . The load resistor now serves two purposes: it limits the current through LED and biases  $Q_3$  when this transistor needs to be driven into saturation. Applying  $IN = 5\text{ V}$  in Fig. 4.9 causes both  $Q_2$  and  $Q_3$  to be in saturation region which produces  $OUT = V_{OL}$ . The resulting  $I_{OL}$  turns on the LED.

$$I_{OL} = \frac{(V_{CC} - V_{LED} - V_{OL})}{R_L} \quad (4.4)$$

Then,  $R_L$  is calculated as


$$R_L = \frac{(V_{CC} - V_{LED} - V_{OL})}{I_{LED}} \quad (4.5)$$

where  $I_{LED} = I_{OL}$ .




### 4.3 Two-Input TTL Nand Logic Gate

Two-input TTL NAND gate is shown in Fig. 4.11. In this figure,  $Q_1$  produces two emitter ports each of which is connected to separate external inputs,  $IN_1$  and  $IN_2$ .

 


**Fig. 4.11** Two-input TTL NAND gate

Figure 4.12 shows both inputs of the two-input TTL NAND gate connected to 0 V. In this figure,  $Q_1$  has been transformed into three discrete diodes,  $D_1$ ,  $D_2$  and  $D_3$ , to make the circuit analysis simpler. When  $IN_1 = IN_2 = 0$  V, both  $D_1$  and  $D_3$  turn on. However, the voltage drop across either diode will not be sufficient to turn on  $D_2$ ,  $Q_2$  and  $Q_3$  as discussed earlier.  $Q_4$  is driven into saturation and supplies  $I_{OH}$  to an output load. The output of the NAND gate transitions to logic 1.

 


**Fig. 4.12** Two-input TTL NAND gate when  $IN_1 = IN_2 = \text{logic } 0$

When one of the inputs of the NAND gate is connected to ground while the other tied to logic 1, only  $D_3$  turns on. Both  $Q_2$  and  $Q_3$  turn off as shown in Fig. 4.13. As a result,  $Q_4$  is driven into saturation and the output transitions to logic 1.

 

**Fig. 4.13** Two-input TTL NAND gate when one of the inputs is at logic 0 ( $IN_2 = \text{logic } 0$ )


When both inputs of the NAND gate are tied to logic 1, both  $D_1$  and  $D_3$  turn off as shown in Fig. 4.14. The current through  $R_1$  saturates  $Q_2$ , and  $Q_2$ 's emitter current saturates  $Q_3$ . The sum of voltage drops across the collector-emitter junction of  $Q_2$  and collector-base junction of  $Q_3$  now reaches about 0.8 V. However, this voltage becomes insufficient to turn on  $Q_4$  and the output diode. As a result, the output terminal is pulled low to about 0.2 V and sinks any current from an external load.

 

**Fig. 4.14** Two-input TTL NAND gate when  $IN_1 = IN_2 = \text{logic } 1$


#### 4.4 Two-Input TTL NOR Logic Gate

Two-input TTL NOR gate is shown in Fig. 4.15. This circuit contains two extra transistors,  $Q_{11}$  and  $Q_{12}$ , at the input, and another two,  $Q_{21}$  and  $Q_{22}$ , at the control stage, to produce the NOR behavior.

 


**Fig. 4.15** Two-input TTL NOR gate

When both  $IN_1$  and  $IN_2$  are grounded, the diodes,  $D_1$  and  $D_3$  corresponding to the emitter-base junctions of  $Q_{11}$  and  $Q_{12}$ , turn on as shown in Fig. 4.16. The voltage drop across either of these diodes will not be sufficient to turn on  $D_2$ ,  $D_4$ ,  $Q_{21}$ ,  $Q_{22}$  and  $Q_3$ . The transistor,  $Q_4$ , goes into saturation because a large current is supplied to the base of this transistor through  $R_2$ . As a result, the emitter current of  $Q_4$  produces a source current to an external load, and the output of the gate is pulled up to logic 1.

 


**Fig. 4.16** Two-input TTL NOR gate when  $IN_1 = IN_2 = \text{logic } 0$

When  $IN_1$  is tied to logic 1 and  $IN_2$  at logic 0 (or vice versa), the diode,  $D_1$  corresponding to the emitter-base of  $Q_{11}$ , turns off because there is 0 V across it as shown in Fig. 4.17.  $Q_{21}$  goes into saturation because a large current is supplied to the base of this transistor through  $R_{11}$  but  $Q_{22}$  stays off. A large portion of  $Q_{21}$ 's emitter saturation current flows into the base of  $Q_3$  and saturates this transistor. In the mean time, the output diode  $D$  and  $Q_4$  turn off, leaving  $Q_3$  in charge of sinking all current from an external load and pulling the output terminal to logic 0.

 

**Fig. 4.17** Two-input TTL NOR gate when one of the inputs is at logic 0 ( $IN_2 = \text{logic } 0$ )

When  $IN_1$  and  $IN_2$  are at logic 1, the diodes,  $D_1$  and  $D_3$  corresponding to the emitter-base junctions of  $Q_{11}$  and  $Q_{12}$ , turn off as shown in Fig. 4.18. However, both  $Q_{21}$  and  $Q_{22}$  go into saturation because of large currents supplied to the base of these transistors through  $R_{11}$  and  $R_{12}$ , respectively. The sum of emitter saturation currents from  $Q_{21}$  and  $Q_{22}$  drive  $Q_3$  into saturation and lower the output voltage to logic 0. Now,  $Q_3$  is able to sink any current from an external load.

 


**Fig. 4.18** Two-input TTL NOR gate when  $IN_1 = IN_2 = \text{logic } 1$
 
#### 4.5 Input Current and Voltage Measurements of a Logic Gate


It is imperative to know the typical values of input and output terminal currents and voltages of a logic gate in order to eliminate potential electrical problems when interconnecting the gate with other gates to implement a logic block. This especially applies to logic gates fabricated using different technologies, i.e. a TTL gate interfacing a CMOS gate or vice versa.

Figure 4.19 shows the schematic to measure the input terminal current,  $I_{IL}$ , and voltage,  $V_{IL}$ , when the input is lowered. The potentiometer connected at the input constantly adjusts the value of  $V_{IL}$  while the resistor,  $R_{PROT}$ , limits the magnitude of  $I_{IL}$ . According to this figure, the minimum and maximum values of  $V_{IL}$  become equal to  $R_{PROT} I_{IL}$  and  $(R_{POT} + R_{PROT}) I_{IL}$ , respectively where  $R_{POT}$  is the maximum potentiometer value.



**Fig. 4.19** Input current ( $I_{IL}$ ) and voltage ( $V_{IL}$ ) measurements when the input voltage is low


Figure 4.20 shows the setup to measure the input current,  $I_{IH}$ , and the voltage,  $V_{IH}$ , when the input voltage is high. The potentiometer constantly adjusts the value of  $V_{IH}$  while  $R_{PROT}$  limits the magnitude of  $I_{IH}$ . The minimum and maximum values of  $V_{IH}$  become equal to  $V_{SUP} - (R_{POT} + R_{PROT}) I_{IH}$  and  $V_{SUP} - R_{PROT} I_{IH}$ , respectively.

 

**Fig. 4.20** Input current ( $I_{IH}$ ) and voltage ( $V_{IH}$ ) measurements when the input voltage is high


#### 4.6 Output Current and Voltage Measurements of a Logic Gate

Current and voltage measurements can also be applied to the output terminals of a logic gate. Figure 4.21 shows the setup to measure the output current,  $I_{OL}$ , and the output voltage,  $V_{OL}$ , when the output is low. Here,  $R_{PROT}$  limits the amount of  $I_{OL}$  while the potentiometer adjusts the value of  $V_{OL}$ . According to this figure, the minimum and maximum  $V_{OL}$  can be calculated as  $V_{SUP} - (R_{POT} + R_{PROT}) I_{OL}$  and  $V_{SUP} - R_{PROT} I_{OL}$ , respectively.

 

**Fig. 4.21** Output current ( $I_{OL}$ ) and voltage ( $V_{OL}$ ) measurements when the output voltage is low

The setup in Fig. 4.22 is used if the output terminal current,  $I_{OH}$ , and the output terminal voltage,  $V_{OH}$ , need to be measured when the output is high. Here,  $R_{PROT}$  limits the amount of  $I_{OH}$  while the potentiometer constantly adjusts the value of  $V_{OH}$ . According to this figure, the minimum and maximum values of  $V_{OH}$  can be calculated as  $R_{PROT} I_{OH}$  and  $(R_{POT} + R_{PROT}) I_{OH}$ , respectively.

 


**Fig. 4.22** Output current ( $I_{OH}$ ) and voltage ( $V_{OH}$ ) measurements when the output voltage is high

 It is very possible to interface an old TTL logic gate with a state-of-the-art CMOS logic gate. Logic level adjustment is a critical when interfacing tasks take place between two different logic families. This is mainly because power supply voltages used in each logic family may be different or each logic family may require different input and output logic levels. When interfacing becomes unavoidable, TTL and CMOS gates can be connected either using a passive device such as a resistor or an active device such as a bipolar transistor.

#### 4.7 TTL-CMOS Interface with a Pull-up Resistor

When a TTL gate drives a CMOS gate, an external pull-up resistor,  $R_{PU}$ , must be added to the interface to be able to switch the CMOS gate.




**Fig. 4.23** A common TTL gate driving a CMOS gate with a pull-up resistor,  $R_{PU}$

Figure 4.23 shows the interface where the TTL inverter input, IN, is at logic 1, and its output produces  $OUT = 0.2\text{ V}$ . TTL does not have any problem to switch the state of the CMOS inverter at this voltage level. The combination of a transient discharge current from the input of the CMOS inverter and a static current through the pull-up resistor,  $I_{PU}$ , determines the maximum sink current value,  $I_{OL}$ , of the TTL inverter as shown in Fig. 4.24. The  $I_{OL}$  of the TTL inverter is fetched from the manufacturer’s datasheet to calculate  $R_{PU}$ . Neglecting  $I_{DIS}$ ,  $I_{OL}$  becomes:

$$I_{OL} \approx I_{PU} = \frac{(5 - V_{OL})}{R_{PU}} = \frac{(5 - 0.2)}{R_{PU}} \tag{4.6}$$


Thus,

$$R_{PU} \approx \frac{4.8}{I_{OL}} \tag{4.7}$$

 

**Fig. 4.24** A common TTL gate driving a CMOS gate with  $R_{PU}$  when TTL input is at logic 1


The CMOS switching becomes an issue when the TTL input is at logic 0 as shown in Fig. 4.25. In this case, the TTL output can produce a voltage in the neighborhood of 3.4–3.5 V. This voltage is more than enough to drive another common TTL gate. However, it may not be sufficient to drive a CMOS gate operating with a 5 V voltage supply. In general, CMOS gates require inputs well above their gate threshold voltage to be able to change the state of their output. Therefore,  $Q_4$  will contribute delivering current to the input capacitance of the CMOS gate up until  $OUT$  reaches at 3.4 V. But, charging the input capacitance of the CMOS gate beyond 3.4 V is performed solely by the current through the pull-up resistor,  $I_{PU}$ , until the voltage across the capacitor eventually reaches 5 V.

 

**Fig. 4.25** A common TTL gate driving a CMOS gate with  $R_{PU}$  when TTL input is at logic 0

**Example 4.3** Assume that a TTL inverter operates with  $V_{CC} = 5V$  and needs to drive several CMOS inverters, all operating with  $V_{DD} = 5V$ . Design a passive interface so the TTL inverter has the capability to drive multiple CMOS inverters.

The DC specifications for both parts are given in Fig. 4.26. According to this table, the TTL inverter cannot drive CMOS inverter(s) because the typical  $V_{OHTTL} = 3.4V$  is less than the minimum value of  $V_{IHCMOS} = 4V$ . Therefore, a pull-up resistor must be included between the gates as a passive interface. The low level voltages are compatible since  $V_{OLTTL} = 0.25V$  is below the maximum  $V_{ILCMOS} = 1V$ .

 

**Fig. 4.26** DC parameter diagram for the TTL and CMOS inverters

When the output of the TTL inverter is at logic 0, one can calculate the minimum value of  $R_{PU}$  using Eq. 4.8.

$$R_{PU} = \frac{(5 - V_{OLTTL})}{I_{OLTTL}} = \frac{(5 - 0.25)}{8\text{mA}} = 593 \Omega \quad (4.8)$$

$R_{PU}$  can be increased as high as 1 K $\Omega$ . However, this produces a static current of  $I_{OLTTL}$  of 4.75 mA while the remaining current, 8 mA – 4.75 mA = 3.25 mA, is reserved to accommodate transient discharge currents from CMOS inverter input capacitor(s).

When the TTL inverter output switches to logic 1 (only about 3.4 V), the additional current to charge input capacitance of CMOS inverter(s) from 3.4 to 5 V will be through  $R_{PU}$ . This passive charge path creates a time constant of  $\tau = R_{PU} C_{CMOS}$  where  $C_{CMOS}$  is the total input capacitance of CMOS inverter(s). Using smaller  $R_{PU}$  values decreases this transient period at the expense of more power consumption.

Another important consideration in the interface design is the output current capability of the TTL inverter. One can compute both the high and low fan-out values,  $N_H$  and  $N_L$ , as follows:

$$N_H = I_{OHTTL}/I_{IHCOS} = 0.4 \text{ mA}/0.1 \mu\text{A} = 4000$$

and


$$N_L = I_{OLTTL}/I_{ILCMOS} = 8 \text{ mA}/0.1 \mu\text{A} = 80,000$$

According to this calculation, the TTL inverter can support up to 4000 CMOS inverters at its output.

---


## 4.8 TTL-CMOS Interface with a Bipolar Transistor

When a TTL gate drives a CMOS gate, an external active device, such as an NPN bipolar transistor shown in Fig. 4.27, can be used to adjust the required input voltage levels for the CMOS gate. However, using an active device, such as an NPN transistor in the interface, also introduces an extra layer of inversion between the TTL and the CMOS gates, requiring design modifications in the original design for correct logic functionality.

 

**Fig. 4.27** A common TTL gate driving a CMOS gate with an NPN bipolar transistor

 When  $IN = 5\text{ V}$  is applied to the TTL input,  $OUT$  becomes  $0.2\text{ V}$ , which turns off the NPN transistor at the TTL-CMOS interface. The supply current,  $I_{CHAR}$ , through  $R_C$  charges the input capacitor of the CMOS gate to  $5\text{ V}$  as shown in Fig. 4.28.

 


**Fig. 4.28** A TTL gate driving a CMOS gate with an NPN when TTL input is at logic 1

Figure 4.29 examines the case when  $IN = 0\text{ V}$  at the TTL inverter's input. The TTL output becomes about  $3.4\text{ V}$ , which is more than enough to saturate the NPN transistor at the interface.



 




**Fig. 4.31** Block diagram of a high voltage TTL device driving CMOS gate(s)

How can one design an interface between the TTL device and the CMOS gate using (a) a passive network and (b) an active NPN bipolar transistor that can transform the voltage levels?

The first task is to use passive elements, such as resistors, at the interface. When the TTL device produces  $V_{OH} = 20V$ , the CMOS gate can only accommodate a maximum of  $V_{IH} = 3V$ . If we use a passive pull-up resistor at the interface for logic translation, the TTL high output voltage appears directly at the input of the CMOS gate and burn the device. Therefore, the only other choice is to use a step-down resistor network composed of  $R_1$  and  $R_2$  as shown in Fig. 4.32.



**Fig. 4.32** Passive interface design when TTL device produces high output

Therefore,

$V_{OH} = (R_1 + R_2) I_{OH}$  since the input impedance of the CMOS gate approaches infinity. Substituting the values of  $V_{OH}$  and  $I_{OH}$  yields:

$$20 \text{ V} = (R_1 + R_2)100 \text{ mA}$$

or

$$R_1 + R_2 = 200 \Omega \quad (4.15)$$

However,

$$V_{IH} = R_2 I_{OH} = 3 \text{ V} \quad (4.16)$$


or

$$R_2 = 30 \Omega \quad (4.17)$$

Thus,

$$R_1 = 200 - 30 = 170 \Omega \quad (4.18)$$

Figure 4.33 shows the opposite case when the TTL output becomes  $V_{OL} = 0 \text{ V}$ , and sinks  $100 \text{ mA}$  current emanating from the interface. However, this case does not provide additional information in calculating anything else but identifying the transient properties of the interface composed of  $I_{OL}$  and the total input capacitance of CMOS gate(s), leading to the calculation of TTL-fanout.

 

**Fig. 4.33** Passive interface design when TTL device produces low output

The result of using resistive network creates a static power consumption of  $I_{OH} V_{OH} = 2 \text{ W}$ , which is quite high to be able to use resistors.

The next design suggests using a NPN bipolar transistor at the interface to adjust the current and voltage levels. However, the inclusion of this device also inverts the TTL output and requires redesigning the logic functionality.

When TTL output produces  $V_{OH} = 20 \text{ V}$  and  $I_{OH} = 100 \text{ mA}$  as shown in the equivalent circuit in Fig. 4.34, the bipolar transistor at the interface goes into saturation.  $I_{BSAT}$  becomes equal to  $I_{OH}$ .

Thus,

$$V_{OH} = R_B I_{BSAT} + V_{BESAT} = R_B I_{OH} + V_{BESAT} \quad (4.19)$$

$$20 - 0.8 = R_B 100 \text{ mA}$$

$$R_B = \frac{19.2}{100 \text{ mA}} = 192 \Omega \quad (4.20)$$

Similarly,

$$V_{SUP} = R_C I_A + V_{CESAT} \quad (4.21)$$

$$I_A \approx I_{CSAT} = \frac{(3 - 0.2)}{R_C} = \frac{2.8}{R_C} \quad (4.22)$$

However, to keep the bipolar transistor in saturation one needs:

$$I_{BSAT} \gg I_{BACT} \quad (4.23)$$

A conservative approach is to make  $I_{BSAT}$  10 times higher than  $I_{BACT}$ . However, the use of smaller multipliers, such as 2 or 3, is possible depending on the transistor output I-V characteristics as discussed earlier. Thus,


$$I_{BSAT} \approx 10 I_{BACT} = 10 \frac{I_{CACT}}{\beta} \quad (4.24)$$

Substituting the values for  $I_{BSAT} = 100 \text{ mA}$ , and  $I_{CACT} \approx I_{CSAT}$ , and Eq. 4.22 into Eq. 4.24 yields:

$$100 \text{ mA} \approx \frac{10}{\beta} \left( \frac{2.8}{R_C} \right) \quad (4.25)$$


For  $\beta = 100$

$$R_C = \frac{10}{100} \left( \frac{2.8}{100 \text{ mA}} \right) = 2.8 \Omega \quad (4.26)$$

 

**Fig. 4.34** Active interface design when TTL device produces high output

Figure 4.35 illustrates the case where the TTL device output produces  $V_{OL} = 0\text{ V}$  and  $I_{OL} = 100\text{ mA}$ , which turns off the bipolar transistor. No further design data can be obtained from this case.

 


**Fig. 4.35** Active interface design when TTL device produces low output

### 4.9 CMOS-TTL Interface with a Pull-Down Resistor

When a CMOS gate drives a TTL gate, the high logic output of the CMOS gate does not create an issue for the input circuitry of the TTL gate. The problem arises only when the output of the CMOS gate needs to lower the input of the TTL gate towards logic 0, and in



 


**Fig. 4.37** CMOS inverter driving a TTL gate with  $R_{PD}$  when CMOS input is at 5 V

When the CMOS input voltage is 0 V, the PMOS transistor of the CMOS gate turns on and exhibits an equivalent resistance,  $R_p$ , as shown in Fig. 4.38. Since the diode corresponding to the emitter-base junction of  $Q_1$  turns off, the output voltage becomes:

$$OUT = \frac{R_{PD}}{R_p + R_{PD}} V_{CC} \tag{4.28}$$


OUT approaches to  $V_{CC} = 5\text{ V}$  as long as  $R_{PD} \gg R_p$ .

 

**Fig. 4.38** CMOS inverter driving a TTL gate with  $R_{PD}$  when CMOS input is at 0 V

### 4.10 CMOS-TTL Interface with a Bipolar Transistor

When a CMOS gate drives a TTL gate, especially with a different supply voltage, it may be prudent to use an NPN transistor at the interface in order to translate the output voltage levels of the CMOS gate for the input voltage levels of the TTL gate as shown in Fig. 4.39. However, the bipolar circuit also creates a logic inversion as indicated previously.

 

**Fig. 4.39** CMOS inverter driving a TTL gate with an NPN bipolar transistor

Figure 4.40 shows when  $IN = 0\text{ V}$  is applied to the input of the CMOS inverter. Since the output of the CMOS inverter reaches 5 V, the NPN transistor at the interface saturates. Therefore, one must satisfy  $I_{BSAT} \gg I_{BACT}$  for this transistor to enter into the saturation region.

Using a conservative multiplication factor of 10,  $I_{BSAT} \approx 10I_{BACT}$ .

Thus,


$$I_{BSAT} \approx 10 \frac{I_{CACT}}{\beta} \quad (4.29)$$

However,

$$I_{BSAT} = I_{OHCOS} \quad (4.30)$$

and

$$I_{CSAT} = I_A + I_{ILTTL} = \frac{(V_{CC} - V_{ILTTL})}{R_C} + I_{ILTTL} \approx I_{CACT} \quad (4.31)$$

 

**Fig. 4.40** CMOS inverter driving a TTL gate with a bipolar transistor when  $IN = 0$  V

Here,  $I_{OHCMS}$  is the high output current of the CMOS gate, and  $V_{ILTTL}$  and  $I_{ILTTL}$  are the low input voltage and input current of the TTL gate, respectively.

Substituting the values of  $I_{BSAT}$  in Eq. 4.30 and  $I_{CSAT} \approx I_{CACT}$  in Eq. 4.29 in Eq. 4.29 yields:

$$I_{OHCMS} = \frac{10}{\beta} \left( \frac{V_{CC} - V_{ILTTL} + R_C I_{ILTTL}}{R_C} \right) \quad (4.32)$$

Reorganizing the terms in Eq. 4.32 yields:

$$R_C = \frac{10(V_{CC} - V_{ILTTL})}{(\beta I_{OHCMS} - 10 I_{ILTTL})} \quad (4.33)$$


$R_B$  is selected as follows:

$$V_{OHCMOS} = R_B I_{BSAT} + 0.8 = R_B I_{OHCMOS} + 0.8 \quad (4.34)$$

Here,  $V_{OHCMOS}$  is the high output voltage of the CMOS gate. Then,

$$R_B = \frac{(V_{OHCMOS} - 0.8)}{I_{OHCMOS}} \quad (4.35)$$

When  $IN = 5\text{ V}$ , the output voltage of the CMOS gate becomes equal to  $V_{OLCMOS}$  as shown in Fig. 4.41. However, this voltage is not sufficient to turn on the interfacial bipolar transistor. Therefore, the NPN transistor's collector reaches  $5\text{ V}$  and turns off the diode corresponding to the emitter-base junction of  $Q_1$  in the TTL gate.

 

**Fig. 4.41** CMOS inverter driving a TTL gate with a bipolar transistor when  $IN = 5\text{ V}$

## Review Questions


1. Determine  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  resistors in a TTL inverter with the following I/O characteristics. Use  $\beta = 100$  for all four NPN transistors. Assume  $V_{CC} = 5\text{ V}$ .

$$\begin{aligned} V_{IL} &= 0.2\text{ V} & V_{OL} &= 0.2\text{ V} \\ V_{IH} &= 3.5\text{ V} & V_{OH} &= 3.5\text{ V} \\ I_{IL} &= 1\text{ mA} & I_{OL} &= 10\text{ mA} \\ I_{IH} &= 0\text{ mA} & I_{OH} &= 10\text{ mA} \end{aligned}$$

2. Determine  $R_1$ ,  $R_2$  and  $R_3$  resistors in an open collector TTL inverter with the following I/O characteristics. Use  $\beta = 100$  for all four NPN transistors. Assume  $V_{CC} = 20\text{ V}$ .

$$\begin{aligned} V_{IL} &= 0.2\text{ V} & V_{OL} &= 0.2\text{ V} \\ V_{IH} &= 20\text{ V} & V_{OH} &= 20\text{ V} \\ I_{IL} &= 1\text{ mA} & I_{OL} &= 10\text{ mA} \\ I_{IH} &= 0\text{ mA} & I_{OH} &= 0\text{ mA} \end{aligned}$$

 3. Implement  $\text{out} = A \oplus B$  in a TTL logic gate using discrete gates. Try to implement the same logic function in an integrated form using a single gate.
4. A CMOS inverter with 3 V power supply needs to be interfaced with a TTL inverter with 12 V power supply as shown below. The interface is an active interface composed of an NPN transistor and resistors operating with 12 V power supply. The NPN bipolar transistor has a current gain of  $\beta = 100$ , and it goes into saturation if  $I_{BSAT} \approx 10I_{BACT}$ . The output current and voltage ratings of the CMOS inverter and input current and voltage ratings of the TTL inverter are shown below. Find the resistor values connected to the base and the collector of the NPN transistor in this active interface. Apply both high (3 V) and low logic values (0 V) at the input of the CMOS gate, and check the voltage levels at the interface.



5. A bipolar circuit with an emitter resistance,  $R_E$ , below is used to feed two CMOS inputs.  $TTL_{OUT}$  port has the following characteristics:

$$V_{OH} = 3.5 \text{ V}$$

$$V_{OL} = 0.2 \text{ V}$$

$$I_{OH} = 20 \text{ mA}$$

$$I_{OL} = 20 \text{ mA}$$

Determine the resistors  $R_B$ ,  $R_C$  and  $R_E$ . What are the current and voltage levels at  $CMOS_{IN1}$  and  $CMOS_{IN2}$  ports? According to your calculations, can  $CMOS_{IN2}$  port be used to change the state of a CMOS gate?

